



Lesson 01

Bipolar Junction Transistors

Interactive Seminar

SCHOOL OF
ENGINEERING

E219
Analogue Electronics

Diode & Bipolar Junction Transistor



Refer to Smartbook Sec 29-1. Read up the section and fill up the blanks below:


- Diode is a semiconductor device that made up of a single PN junction
- Diode has 2 terminals, named as **(A)node**, & **(K)Cathode**



- Is Bipolar Junction transistor (BJT) a semiconductor device?
- How many PN junction does BJT has?
- Why is Q_1 a NPN type BJT?
- How is the 3 BJT terminals label as Base**(B)**, Collector**(C)** & Emitter **(E)**?

Biasing a NPN BJT

Refer to Smartbook Sec 29-2

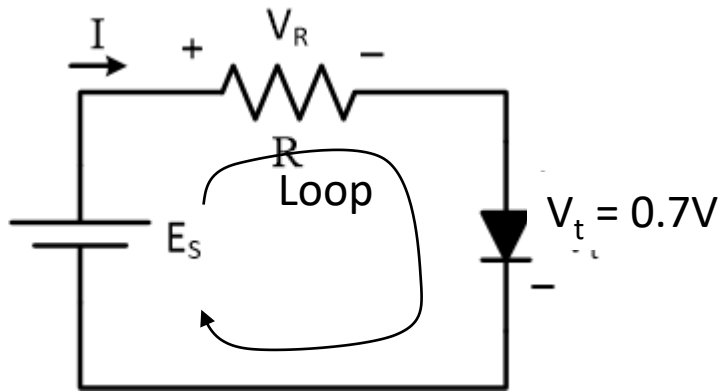

Diode Bias Circuit

- External Voltage Source to bias a Diode circuit


$$E_S = V_R + V_t$$

$$E_S > V_t$$

- What is the difference between BJT biased Circuit and a Diode biased circuit?

- What is the difference between Figure 29-4 of the smartbook and the circuit shown on the left?

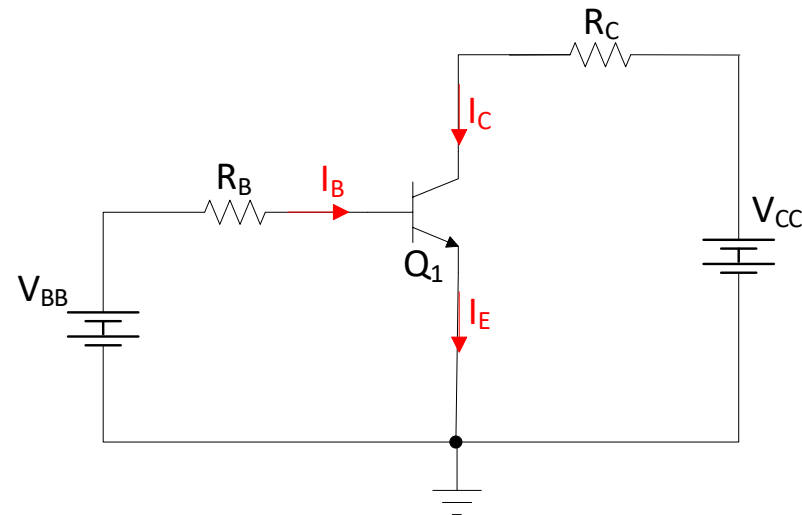- What is the purpose of having a V_{BB} ?



BJT Bias Circuit

Important: All currents shown in Smartbook is electron flow while the currents used in E219 is conventional flow

Biasing a NPN BJT



Refer to Smartbook Sec 29-2, Figure 29-5,


External Voltage Source(s) is needed to provide currents through different parts of the BJT

External DC sources

- V_{BB} : Base Supply Voltage
- V_{CC} : Collector Supply Voltage

Node voltages at BJT terminals

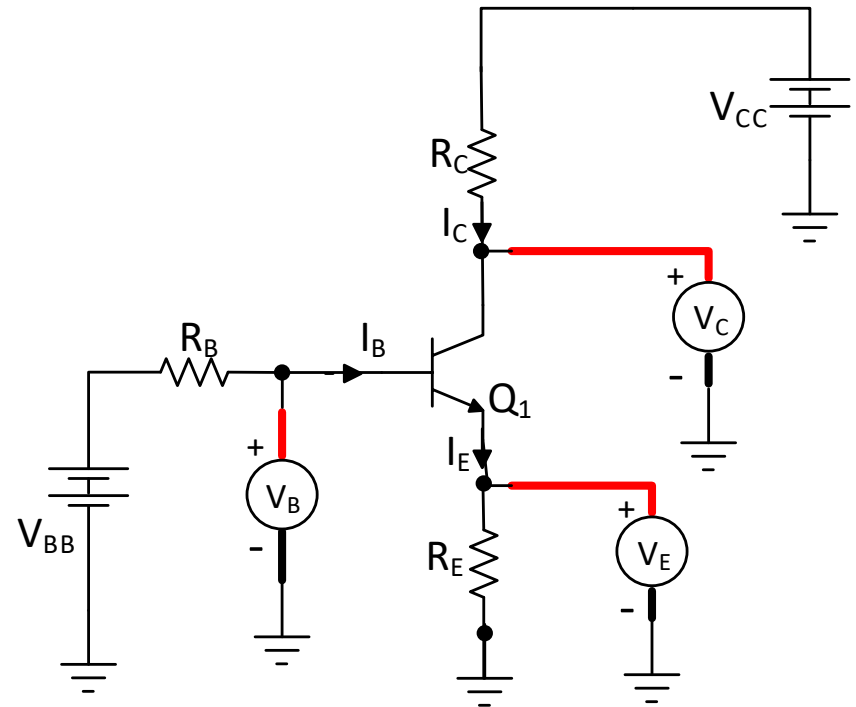
- V_B : Node Voltage at Base
- V_C : Node Voltage at Collector
- V_E : Node Voltage at Emitter



Important Note: **Node Voltage** is measured voltage between the given node and ground

BJT Voltages

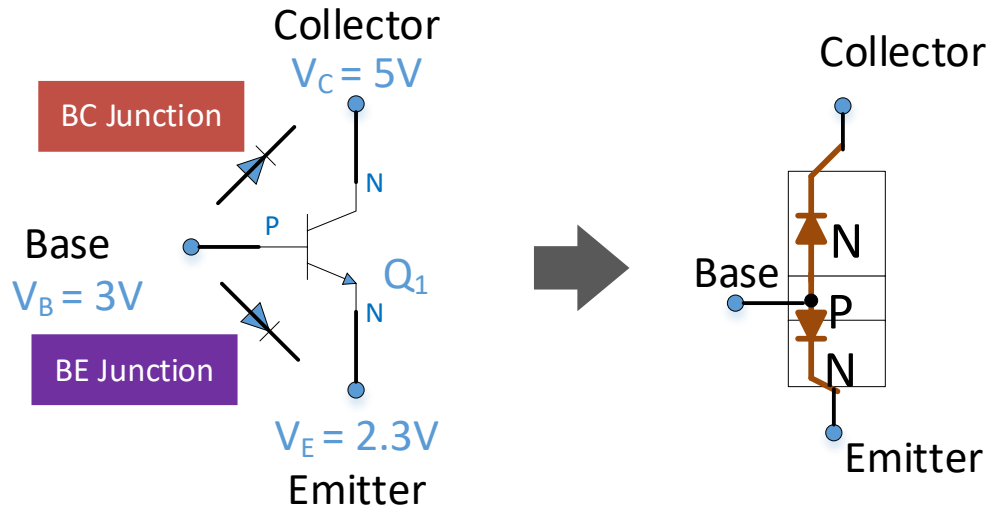Calculation of voltage across two terminals using node voltages



A transistor behaves like two back-to-back diodes : one between terminal B and E, another between terminal B and C.

Typically Forward Bias in a Junction diode $\approx 0.7V$ unless stated otherwise

Voltage across BE terminal

$$V_{BE} = V_B - V_E$$

$$V_{BE} = \boxed{}$$

Voltage across BC terminal

$$V_{BC} = V_B - V_C$$

$$V_{BC} = \boxed{}$$

Voltage across CE terminal

$$V_{CE} = V_C - V_E$$

$$V_{CE} = \boxed{}$$

*Circle the appropriate **Bias Condition** for the respective junction diodes*

BE Junction : Forward / Reverse Bias

BC Junction : Forward / Reverse Bias

BJT Currents

Refer to Smartbook Sec 29-2



- If BE junction is forward biased, currents flow in BJT
 - ✓ I_B is very small
 - ✓ $I_C \approx I_E$
- Based on conventional current flow

By Kirchhoff Current Law (KCL):



$$I_E = I_B + I_C$$

- DC beta, $\beta_{DC} = I_C / I_B$**

DC beta, β_{DC} for $Q_1 =$

- DC alpha, α_{DC} is the ratio of I_C to I_E**

DC alpha, α_{DC} for $Q_1 =$

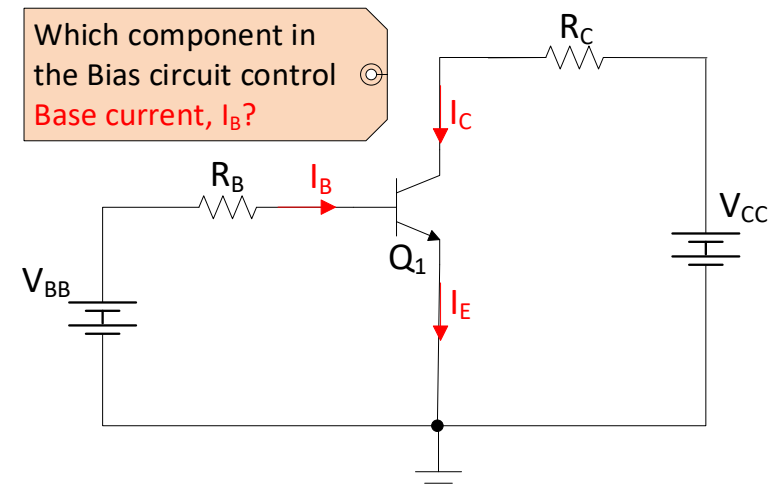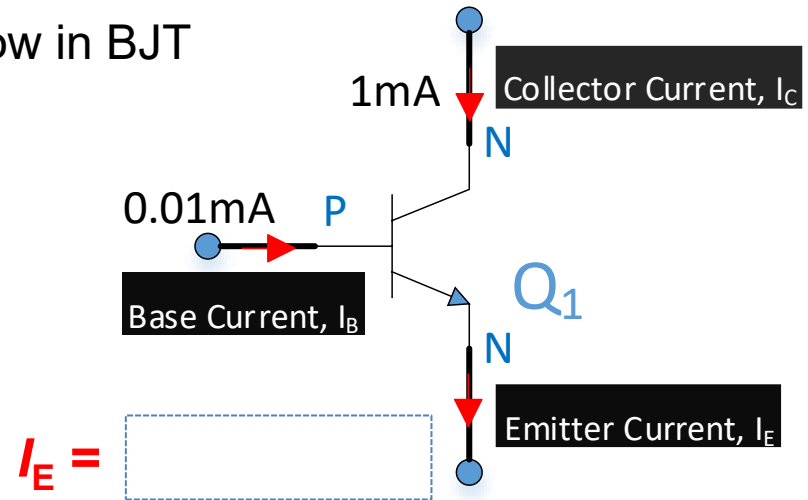


BJT Bias Circuit

BJT - A Non-Linear Device




Recap I-V characteristics of Resistor and Diode

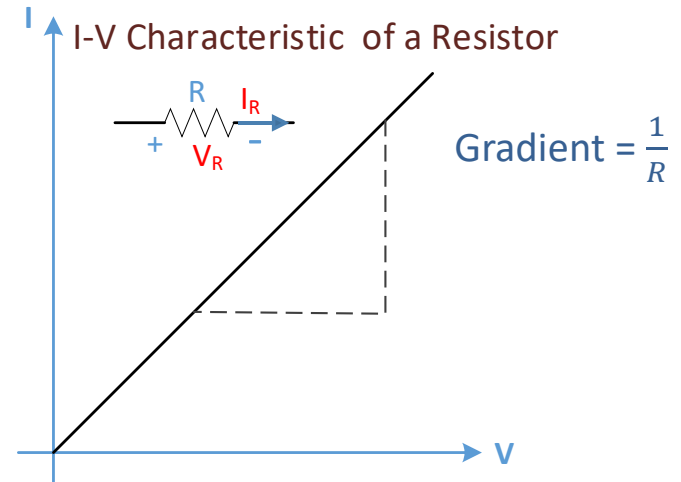
- Resistor is a **linear** device.
- For a fixed R , $V_R \propto I_R$



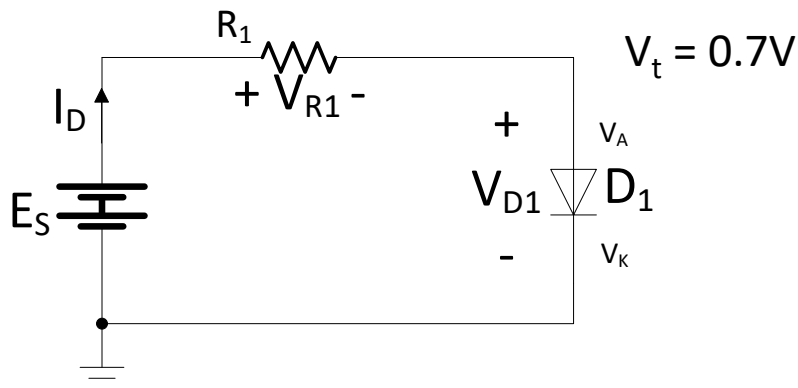- Is Diode a **linear** device?
- When does current starts to flow through D_1 ?
- Which component limits the current flow?



I_D - V_D Characteristic Curve of Diode

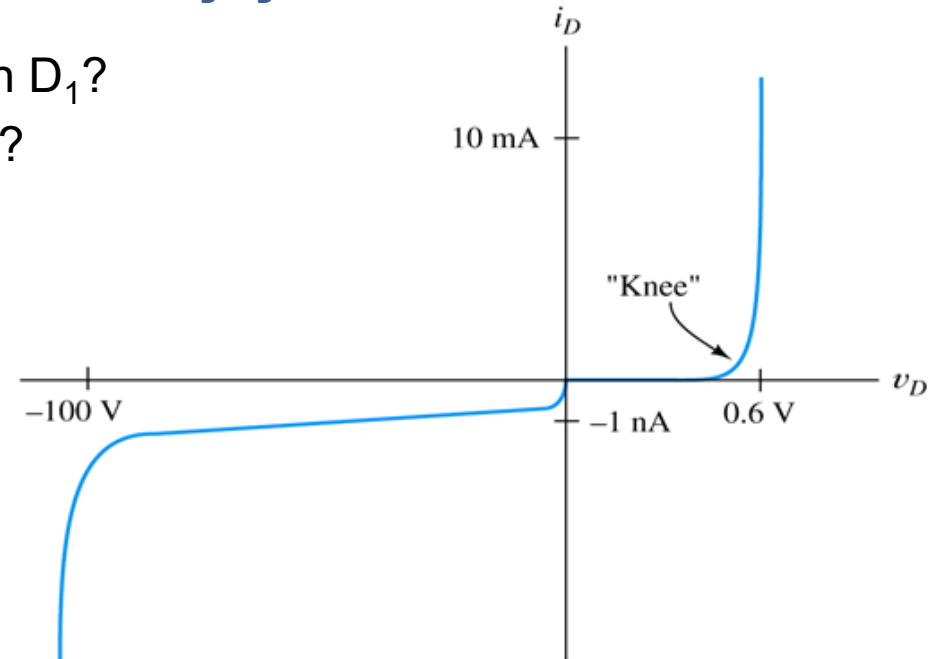

BJT Operation mode : Cut-off Mode

Refer to Smartbook Sec 29-3



- BJT is “fully off”
 - ✓ I_B is very small
 - ✓ $I_C \approx 0A$
- Terminal C-E behaves like Open Circuit

BJT Operation Mode	B-E Junction	B-C Junction
Cut-off	Reverse Bias	Reverse Bias
Active	Forward Bias	Reverse Bias
Saturation	Forward Bias	Forward Bias

BC Junction is

Biased

$$V_{BC} = V_B - V_C$$



$$V_{BC} =$$

BE Junction is

Biased

$$V_{BE} = V_B - V_E$$

$$V_{BE} =$$

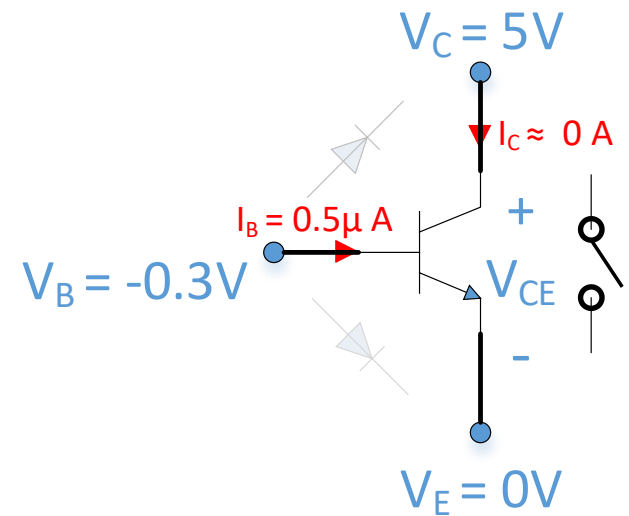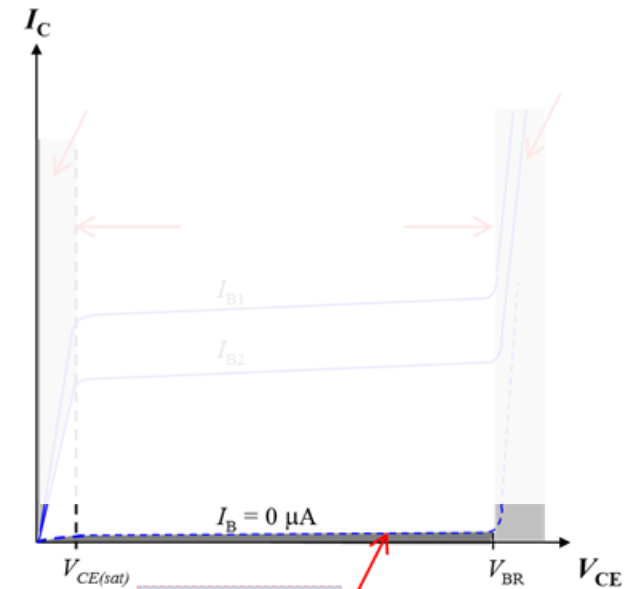


BJT Operation mode : Saturation Mode

Refer to Smartbook Sec 29-3



- BJT is “fully on”
 - ✓ $\beta_{DC} \neq \frac{I_C}{I_B}$
 - ✓ $V_{CE} \leq 0.2V$
- Terminal C-E behaves like Short Circuit

BJT Operation Mode	B-E Junction	B-C Junction
Cut-off	Reverse Bias	Reverse Bias
Active	Forward Bias	Reverse Bias
Saturation	Forward Bias	Forward Bias

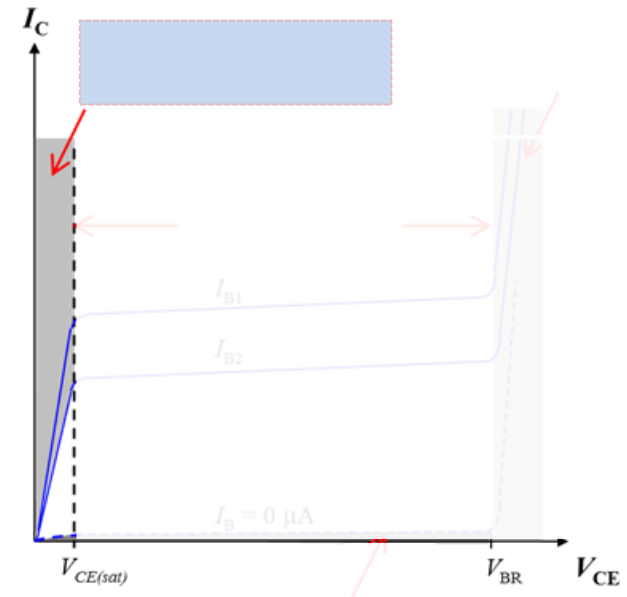

BC Junction is

Biased

$$V_{BC} = V_B - V_C$$


$$V_{BC} =$$

BE Junction is

Biased

$$V_{BE} = V_B - V_E$$

$$V_{BE} =$$

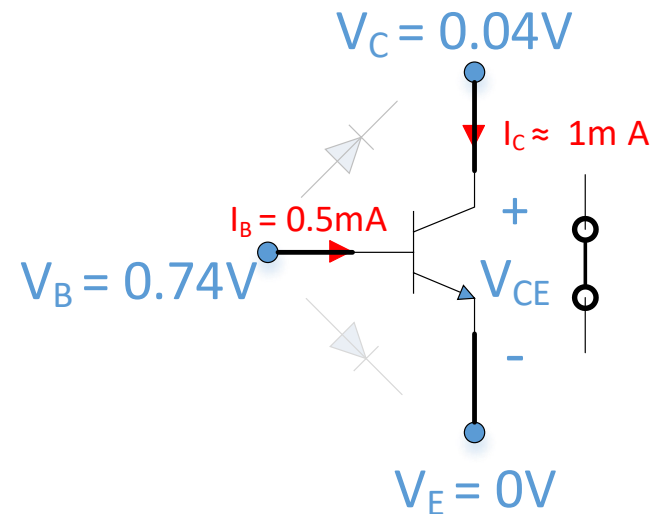


BJT Operation mode : Active Mode

Refer to Smartbook 29-3



- BJT is "Partially on"
 - ✓ $I_C = \beta_{DC} \times I_B$
 - ✓ β_{DC} remains constant regardless of different I_B

BJT Operation Mode	B-E Junction	B-C Junction
Cut-off	Reverse Bias	Reverse Bias
Active	Forward Bias	Reverse Bias
Saturation	Forward Bias	Forward Bias

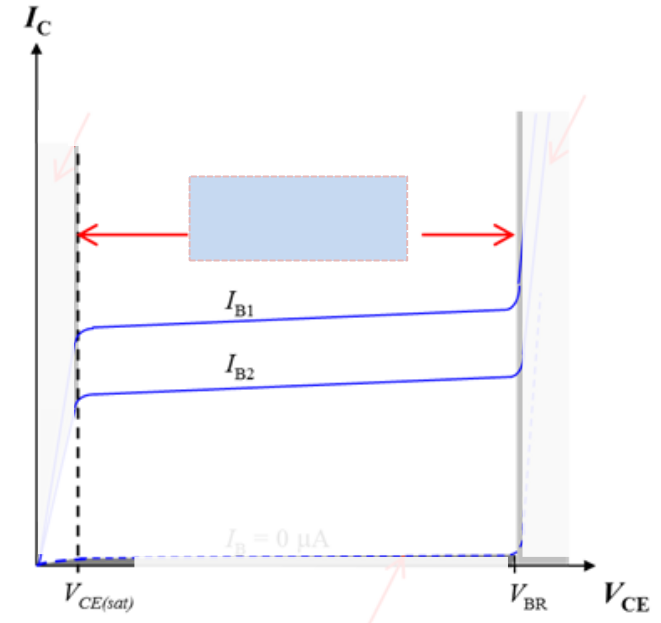

BC Junction is

Biased

$$V_{BC} = V_B - V_C$$


$$V_{BC} =$$

BE Junction is

Biased

$$V_{BE} = V_B - V_E$$

$$V_{BE} =$$

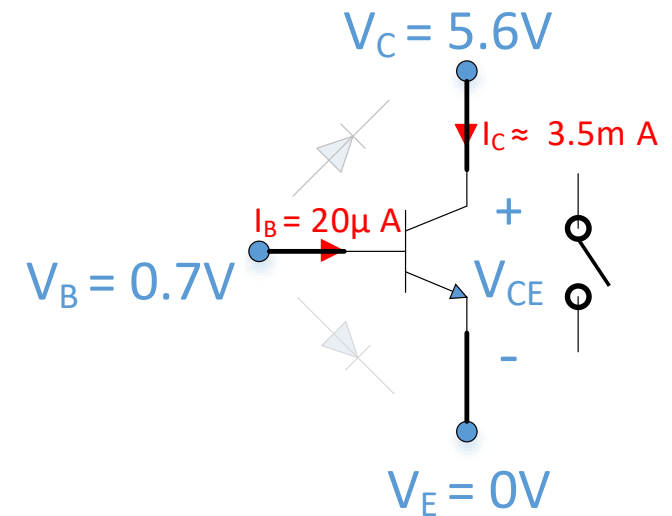

Practice 1

PNP BJT Currents and Voltages



PNP is the complement of NPN BJT


KCL of BJT current remains the same **except** that the **current direction is opposite**

By KCL:

$$I_E = I_B + I_C$$

Take note that the **2 PN junctions of PNP are reverse**

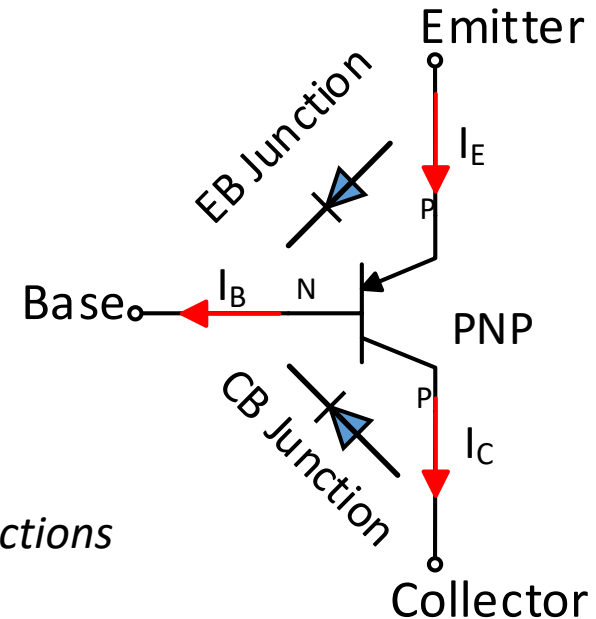In NPN, the 2 PN junctions are BE-Junctions and BC junctions



Circle the appropriate bias condition for different operating modes of a PNP

BJT Mode Of Operation	E-B Junction	C-B Junction
Cut-off	Forward / Reverse Bias	Forward / Reverse Bias
Active	Forward / Reverse Bias	Forward / Reverse Bias
Saturation	Forward / Reverse Bias	Forward / Reverse Bias

Note: *there are no difference in the bias condition for the 3 operation mode regardless of PNP or NPN*


I_C - V_{CE} Characteristic Curve of PNP



- Similar to NPN, small increase in I_B of a PNP generates a large increase in I_C during active operating mode :

$$I_C = \beta_{DC} I_B$$

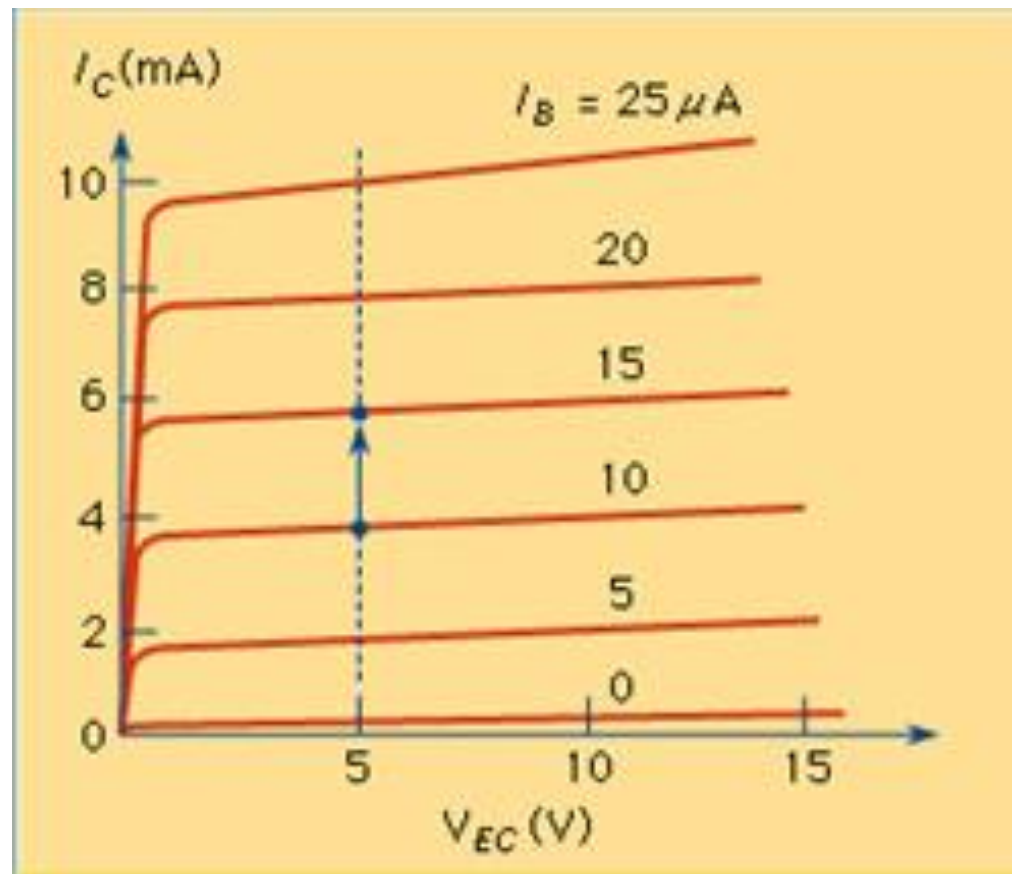Is β_{DC} value the same in Active and Saturation operating Mode?



I_C - V_{EC} Characteristic Curve of PNP

Practice 2



Learning Outcomes



- Describe the basic structure of a BJT
- Differentiate between two types of BJT: PNP; NPN and recognize the electrical symbol of each BJT
- Describe the I-V characteristics and parameters for a BJT
- Explain the various BJT operation region/mode: Cut-off; Active; Saturation
- Explain the effect on the junction currents I_B , I_C , I_E and junction voltages V_B , V_C by external parameters such as V_{BB} , V_{CC} , R_B , R_C .

Useful References



1) Transistors, how do they work?

<https://www.youtube.com/watch?v=7ukDKVHnac4&t=3s>

2) What is transistor?

<https://www.linkedin.com/learning/electronics-foundations-semiconductor-devices/what-is-a-transistor?u=41614228>