

Prefix & Notation

Metric Prefix	Prefix	Engineering Notation
Tera	T	10^{12}
Giga	G	10^9
Mega	M	10^6
Kilo	K	10^3
Milli	m	10^{-3}
Micro	μ	10^{-6}
Nano	n	10^{-9}
Pico	P	10^{-12}

Scientific notation

$$a \times 10^b$$

where $1 \leq a < 10$, b is non-zero integer, can be either positive or negative

Engineering notation

$$a \times 10^b$$

where $0 \leq a$, b can be either positive or negative but **must be multiple of 3**.

Engineering Prefix (notation)

substitute a prefix in place of the x10 and exponent in engineering notation.





Number	Scientific Notation	Engineering Notation	Engineering Prefix Notation
0.046577	4.6577×10^{-2}	0.46577×10^{-3}	0.46577 m
0.0000578321	5.78321×10^{-5}	57.8321×10^{-6}	57.8321 μ
349.8	3.498×10^2	0.3498×10^3	0.3498 K
54945256.8	5.49452568×10^7	54.9452568×10^6	54.9452568 M

SI Units





Parameter	Symbol	SI Unit
Voltage	V	Volt (V)
Current	I	Ampere (A)
Resistance	R	Ohm (Ω)
Power	P	Watts (W)
Capacitance	C	Farad (F)
Inductance	L	Henry (H)
Impedance	Z	Ohm (Ω)
Charge	Q	Coulomb (C)
Frequency	f	Hertz (Hz)
Period	T	Second (s)
Angular Frequency	ω	Rad/s

Parameter	Symbol	SI Unit
Magnetic Flux	Φ	Weber (Wb)
Magnetic Flux Density	B	Tesla (T) or Wb/m ²
Magnetomotive Force	mmf	<i>Ampere Turns (At)</i>
Reluctance	R	<i>(At/Wb)</i>
Permeability of free space	μ_0	<i>Wb/(At.m)</i>
Relative Permeability	μ_r	No unit
Permeability of material	$\mu_m = \mu_0 \mu_r$	<i>Wb/(At.m)</i>
Permittivity of free space	ϵ_0	Farad per meter (F/m)
Relative permittivity	ϵ_r	No Unit
Time Constant	τ	Second (s)

Electromagnetic Induction

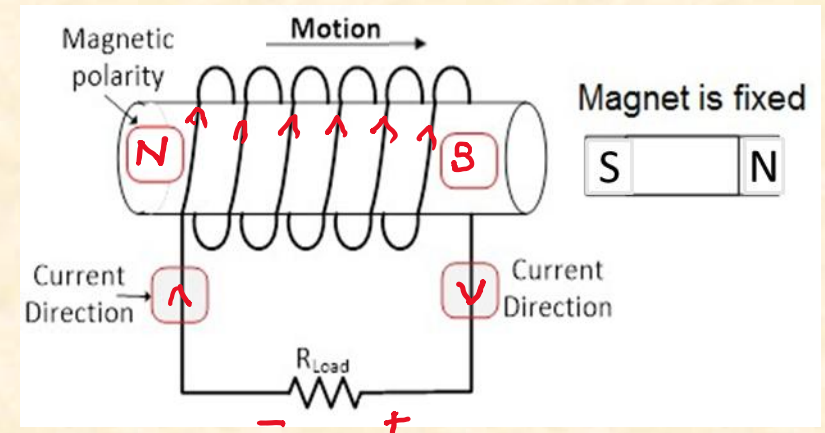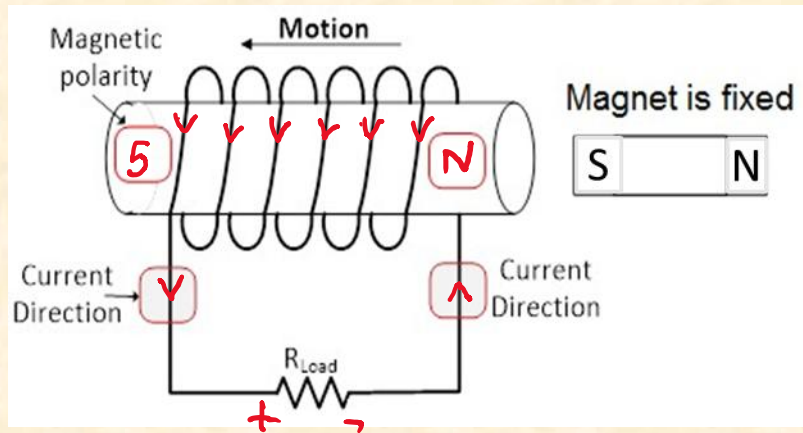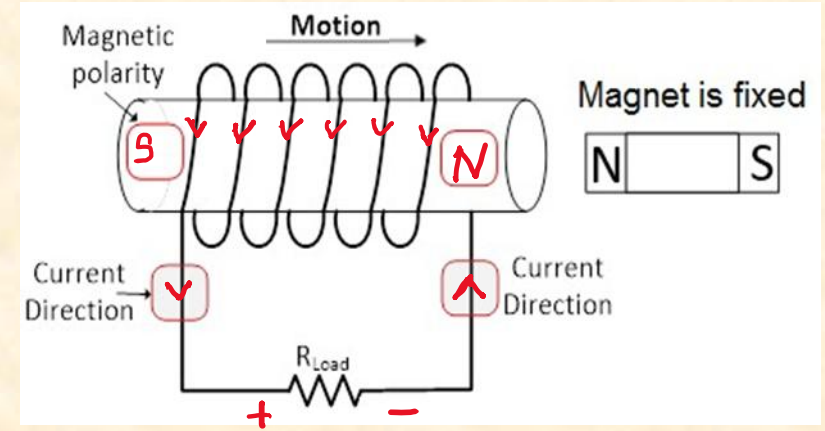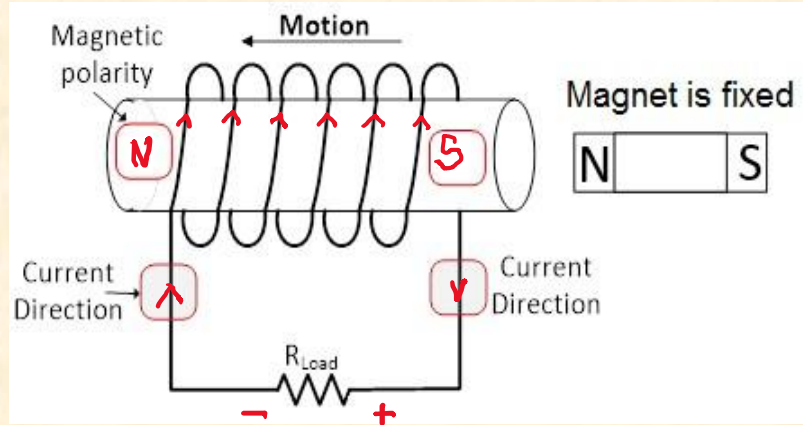

Electromagnetic Induction

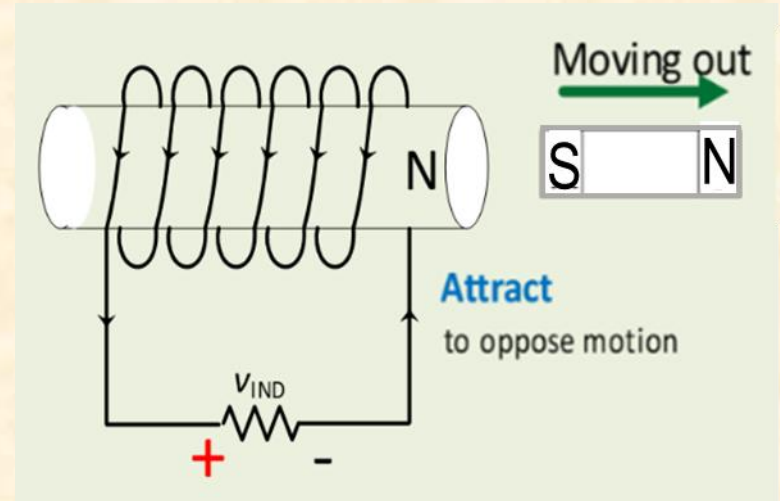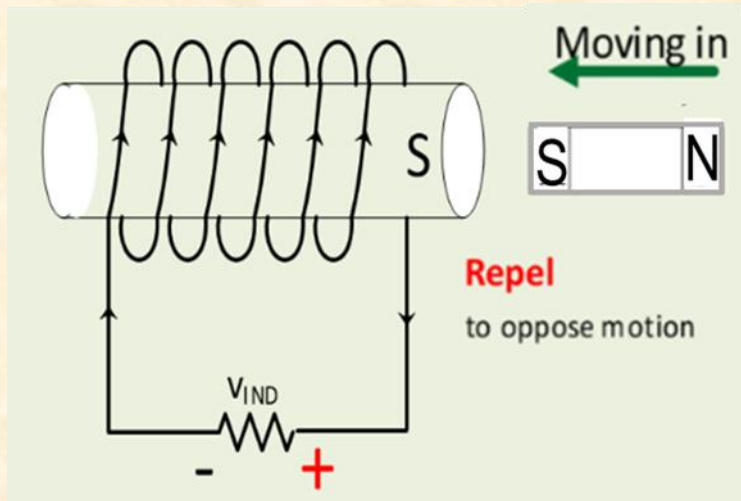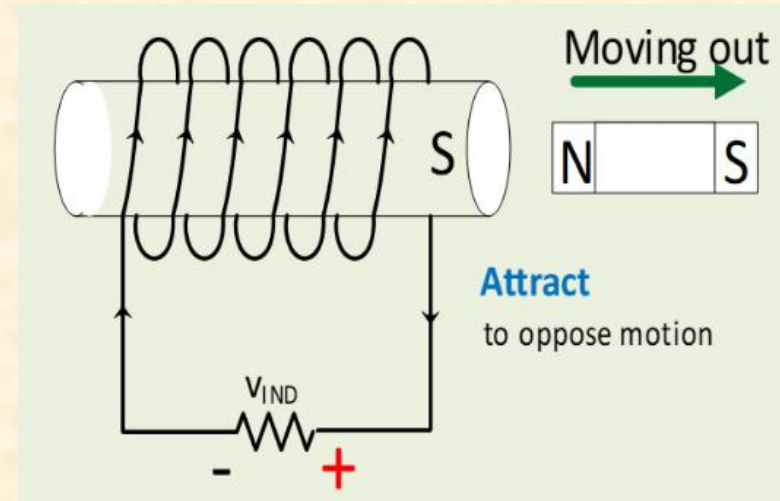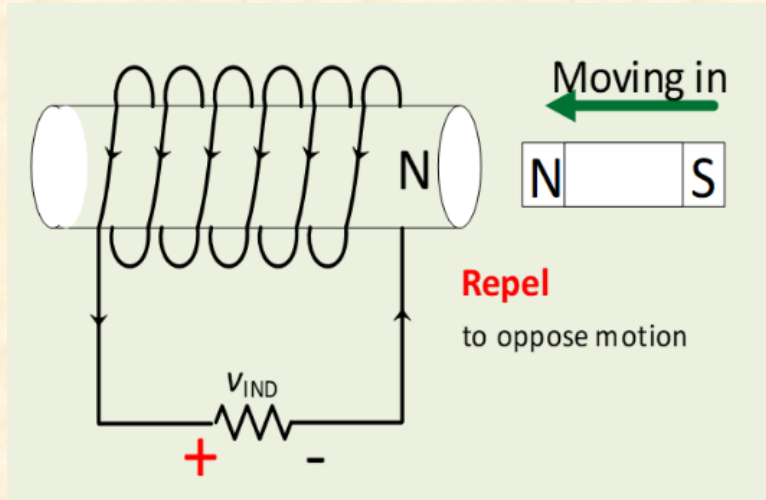


Superposition Theorem


- The analysis of a circuit with **more than one source** can be determined by examining the **individual** contribution from each **source**.
- **All sources except one** must be “**turned off**” and evaluate the circuit currents and voltages.
- The **Final Step** is to determine the total voltage(or current) in any part of a circuit is **equal to the algebraic sum** of the voltages(or currents) produced by each source.

How to “turned off” the voltage & current sources

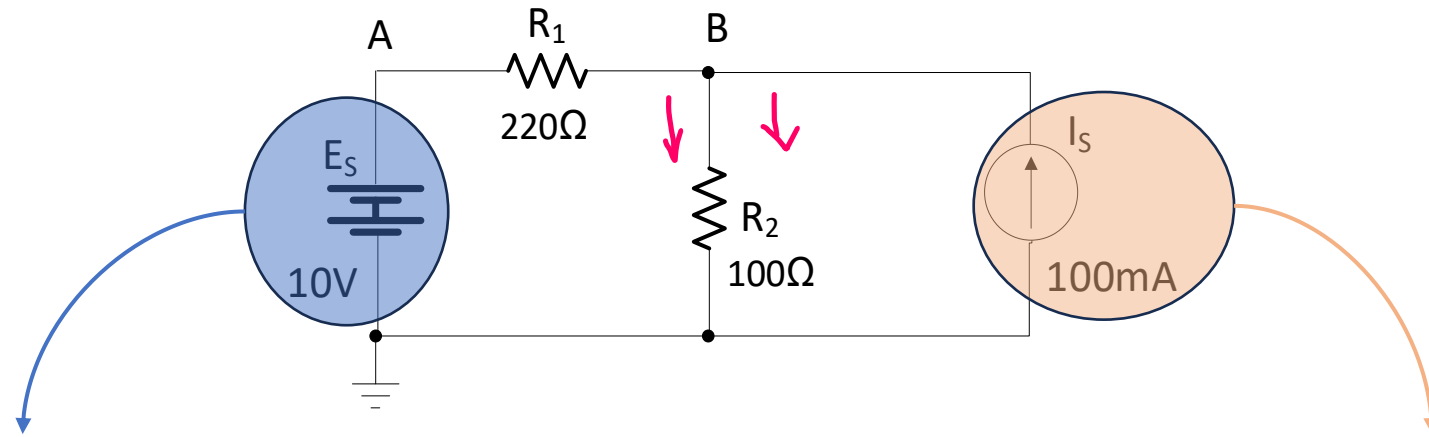
turned off ➡ make zero voltage/current source




$$E_S = V_{AB} = 0V$$

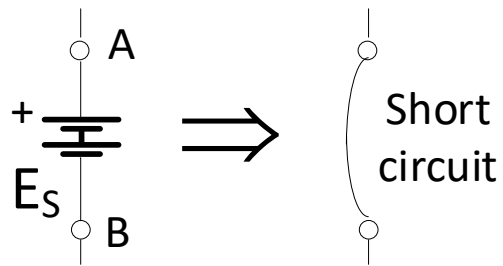

$$I_S = 0A$$

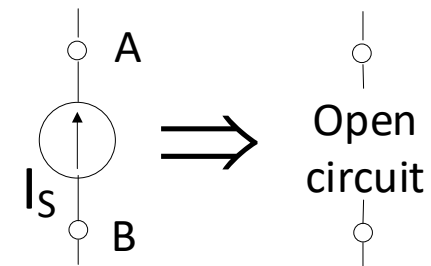

Q2a)

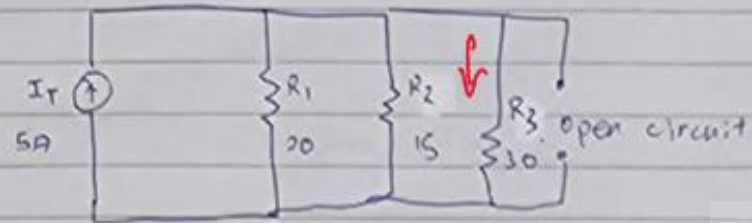

$$R_{EQ} = \frac{1}{\frac{1}{20} + \frac{1}{15} + \frac{1}{30}}$$

$$= 6.67 \Omega$$

$$I_3' = \frac{6.67}{30} \times 5$$

$$= 1.11 \text{ A (2dp)}$$

$\downarrow$

current direction


$(\uparrow)$ or $(\downarrow)$ or $(\rightarrow)$ or $(\leftarrow)$

voltage polarity

$(\begin{smallmatrix} + \\ - \end{smallmatrix})$ $(\begin{smallmatrix} - \\ + \end{smallmatrix})$ $(+ -)$ $(- +)$

+ on top + below + on left + on right

Q2b)

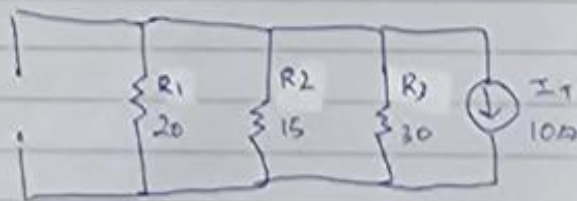

$$I_3'' = \frac{6.67}{30} \times 10$$

$$= 2.22 \text{ A (2dp)}$$

$\uparrow$

$$3a) I_3 = I_3'' - I_3'$$


$$= 2.22 - 1.11$$

$$= 1.11 \text{ A}$$

$\uparrow$

Thevenin's Theorem

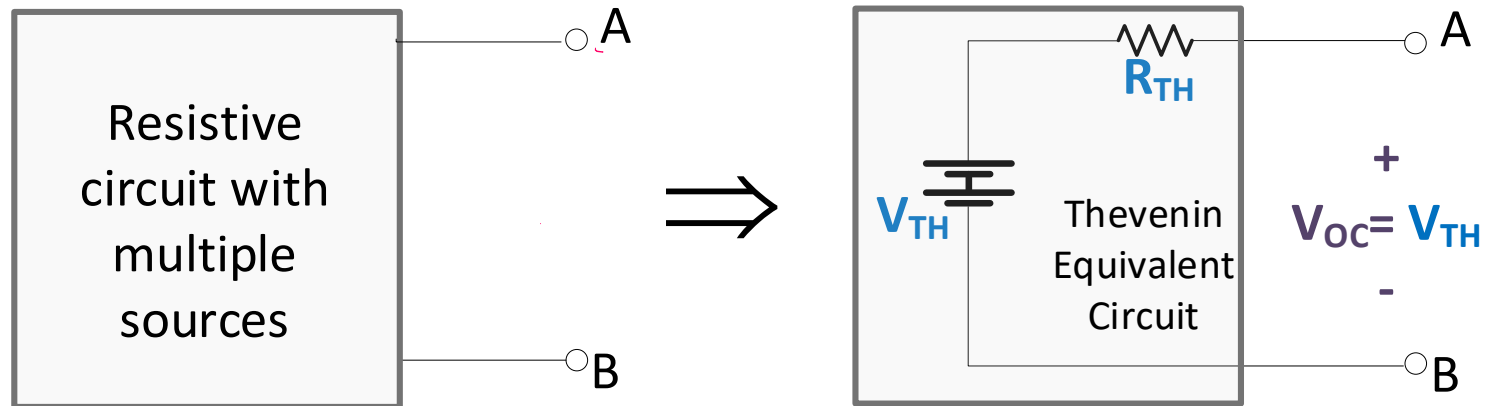
Thevenin's theorem states that any resistive circuit network, can be replaced by voltage source in series with a source resistance when viewed from the output terminals A-B.



A Thevenin's Equivalent Circuit consists of:

- Voltage Source: **Thevenin Voltage, V_{TH}**
- Series Resistance: **Thevenin Resistance, R_{TH}**
- As there is an open circuit between terminal A-B, hence, voltage at the open terminal is known as **Open-Circuit Voltage (V_{OC})**


To find Thevenin's voltage, V_{TH}

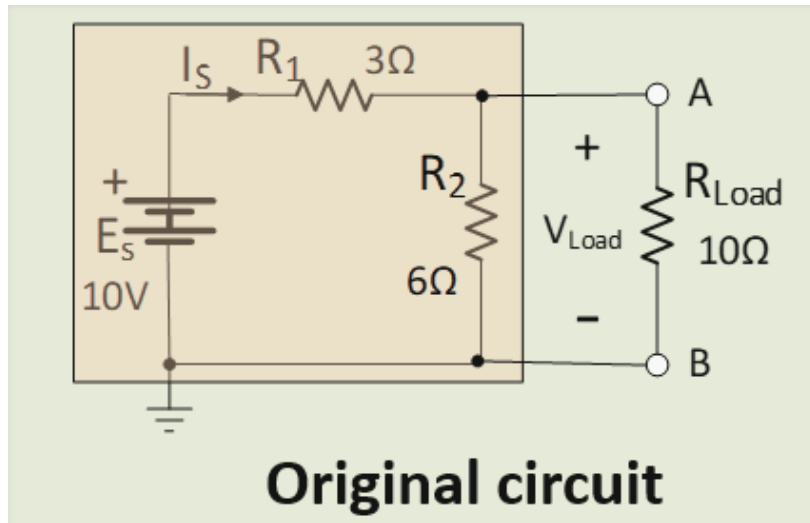

Step 1 : Remove any load/resistor between terminal A-B

Step 2 : Use any appropriate circuit analysis method to find voltage value of VOC

To find Thevenin's Resistance, R_{TH}


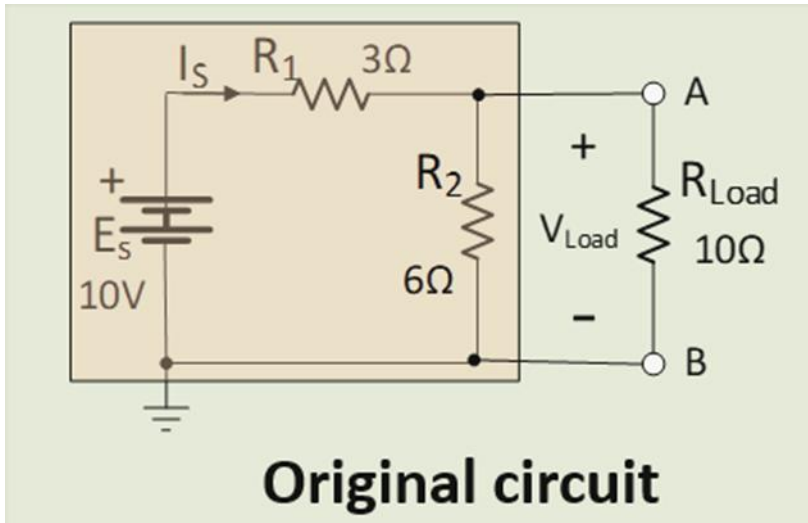


Step 1 : Remove any load/resistor between terminal A-B

Step 2 : Turn off (zero) all the sources (similar methods used in Superposition Theorem)

Step 3 : Find the equivalent resistance, R_{EQ} across the terminal A-B


To draw Thevenin's Equivalent Circuit

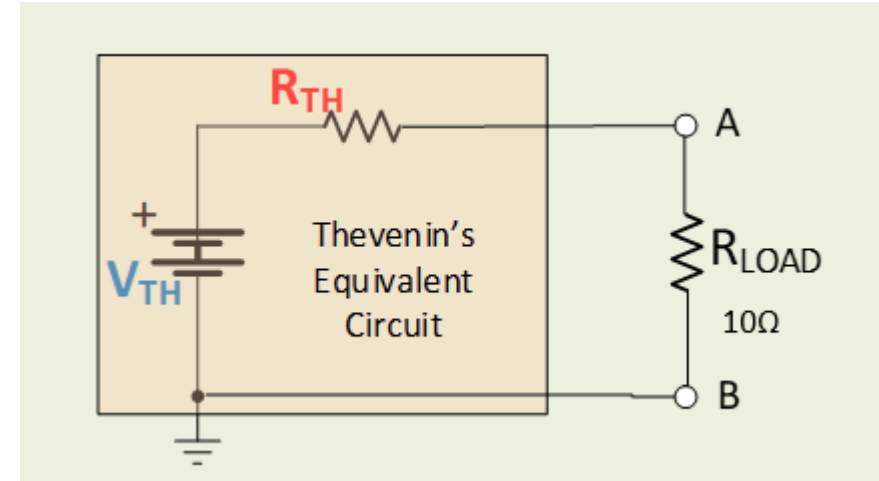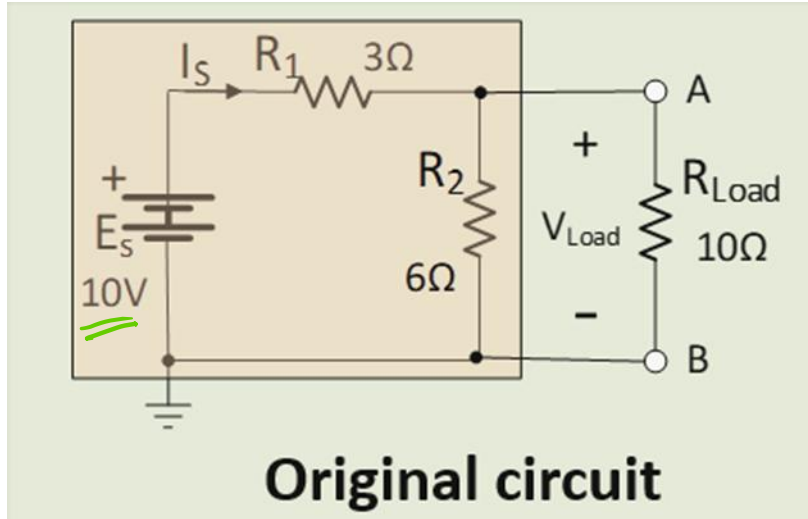

Step 1 : Draw the Thevenin's Equivalent Circuit with the load, R_{LOAD} , **re-connected** to terminal A-B


Step 2 : Analyse voltage and current for the load resistor, R_{LOAD} , when connected back to Thevenin's Equivalent Circuit.

To find Thevenin's voltage, V_{TH}

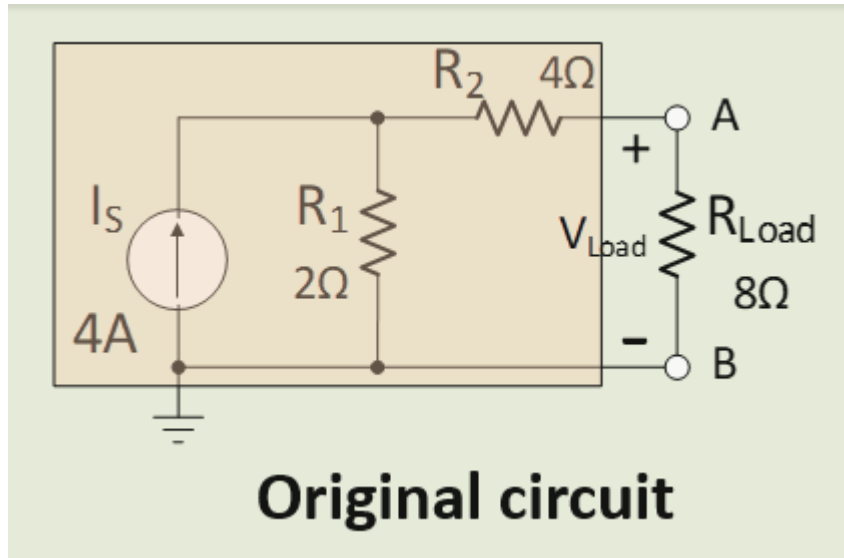


Step 1 : Remove any load/resistor between terminal A-B

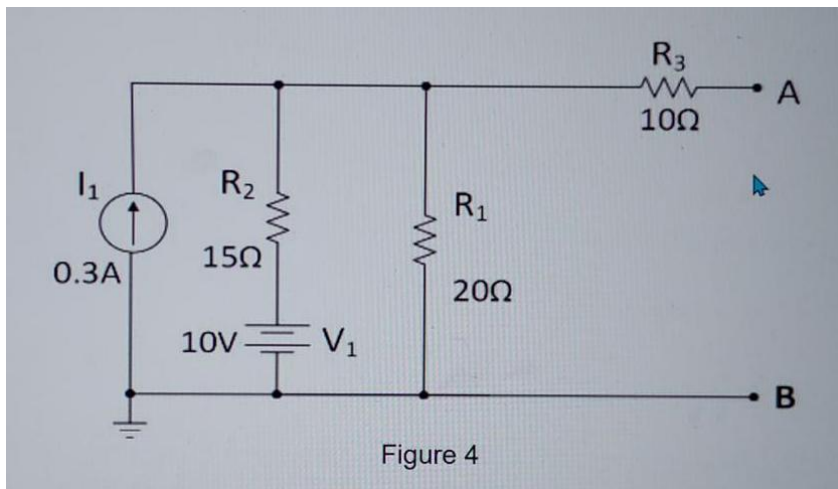Step 2 : Use any appropriate circuit analysis method to find voltage value of VOC



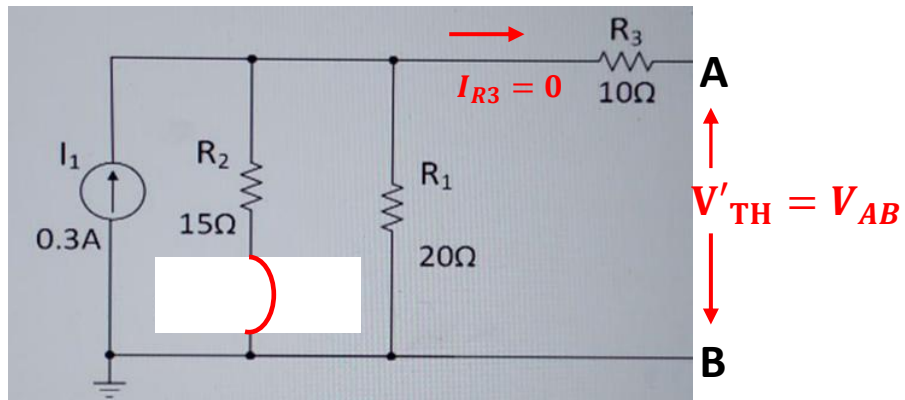
Apply Superposition Theorem to determine **Thevenin Equivalent Voltage, V_{TH}** & **Thevenin Equivalent Resistance R_{TH}** between node A & B.



I_1 splits into R_2 and R_1 . Hence use current divider.

$$I_{R1} = \frac{R_{EQ}}{R_1} \times I_1 \rightarrow R_{EQ} = R_{12}$$
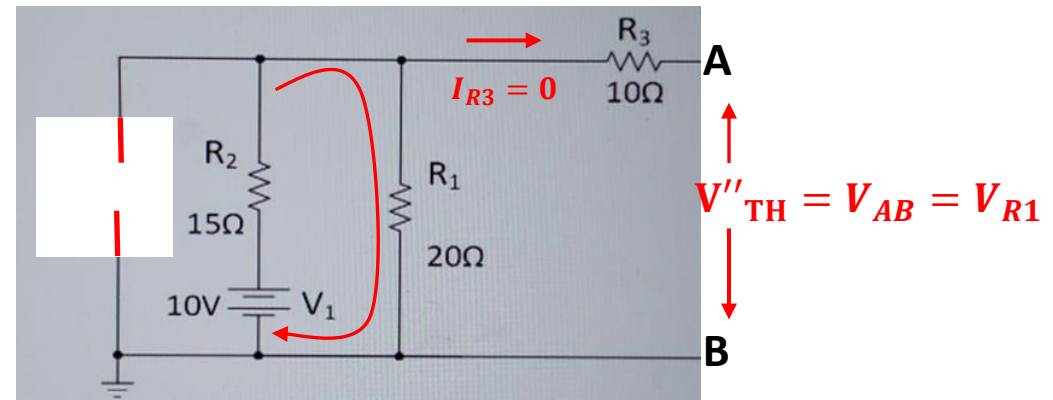
$$V'_{TH} = V_{AB} = V_{R1} + \cancel{V_{R3}^0} = I_{R1} \times R_1$$




Series circuit, current the same. Hence use voltage divider.

$$V_{R1} = \frac{R_1}{R_T} \times V_1$$


$$V_{R1} V_{AB} = V_{R1} + \cancel{V_{R3}^0} = V_{R1}$$

$$V_{TH} = V'_{TH} + V''_{TH}$$

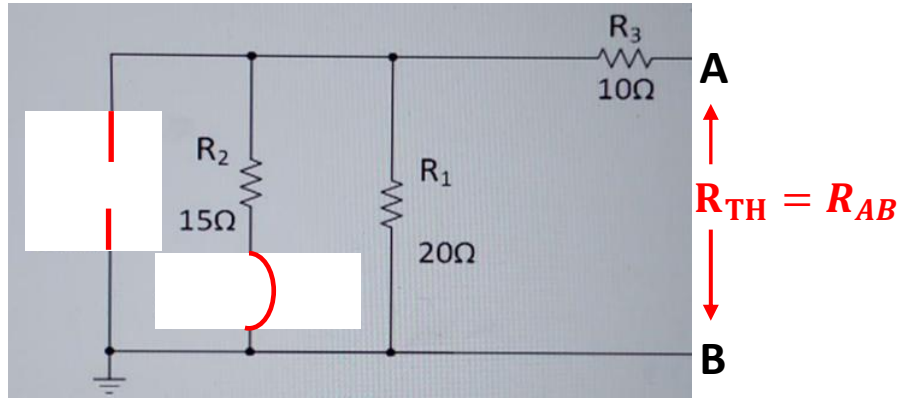

To find R_{TH} , all sources must be turned "OFF"

$$R_{TH} = R_3 + R_1 // R_2$$

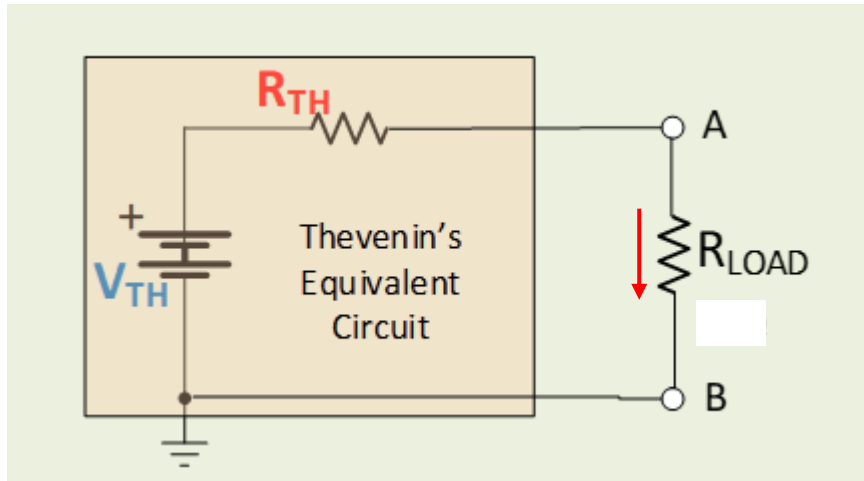

$$V_{R_{Load}} = \frac{R_{Load}}{R_{Total}} \times V_{TH}$$


$$I_{Load} = \frac{V_{R_{load}}}{R_{Load}}$$

Capacitor


- The capacitance of a parallel-plate capacitor is defined by the equation,

$$C = \epsilon_0 \epsilon_r \frac{A}{d} \quad (F)$$

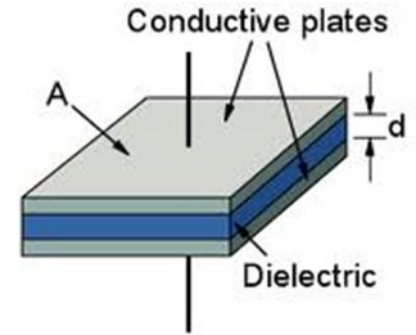ϵ_0 = permittivity of free space $\approx 8.85 \times 10^{-12} F/m$
 ϵ_r = relative permittivity of the dielectric material
 A = area of the plates, m^2
 d = distance between 2 plates




Capacitor in parallel

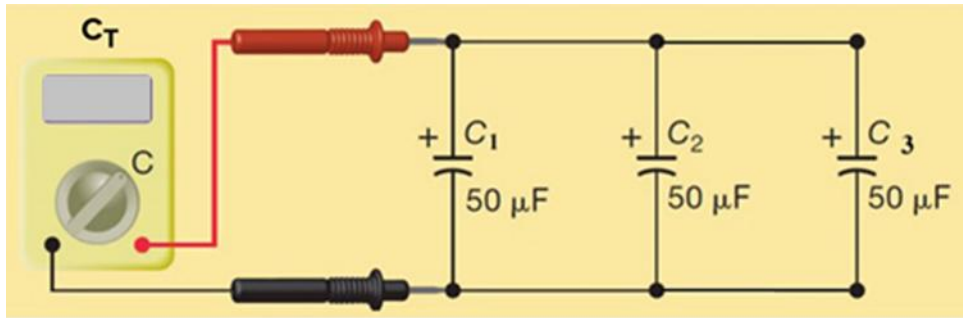


$$C_T = C_1 + C_2 + \dots + C_n$$

Capacitor in series
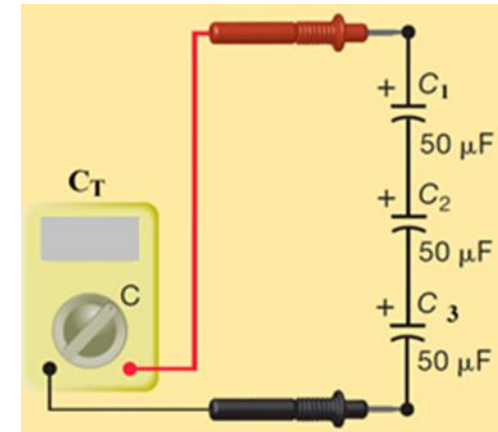
$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$



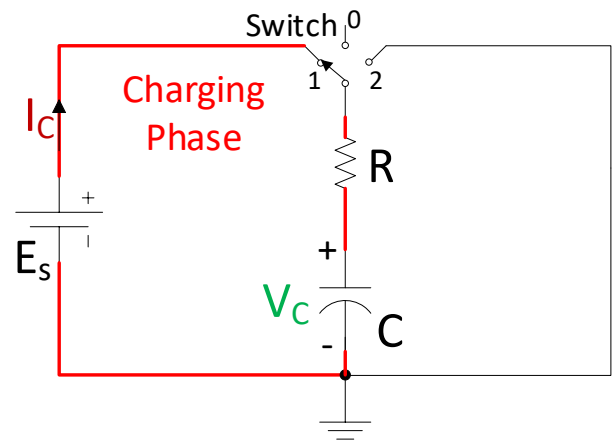Transient curves for series RC circuits - Charging phase



The Time Constant (τ) = $R * C$

Capacitor Voltage V_C

Initial Value = 0 V

Final steady Value = E_S


Capacitor Current I_C

Initial Value = $\frac{E_S}{R}$


Final steady Value = 0 A

Note : $i_C(t) = C \frac{dv}{dt}$,
 i_C is max when $(\frac{dv}{dt})$ is max, i.e $V_C = 0$ at $t=0$

Time Constant τ	Capacitor Voltage V_C	Resistor Voltage V_R
1τ	$0.632 * E_S$	$0.368 * E_S$
2τ	$0.865 * E_S$	$0.135 * E_S$
3τ	$0.95 * E_S$	$0.05 * E_S$
4τ	$0.982 * E_S$	$0.018 * E_S$
5τ	$0.993 * E_S$	$0.007 * E_S$

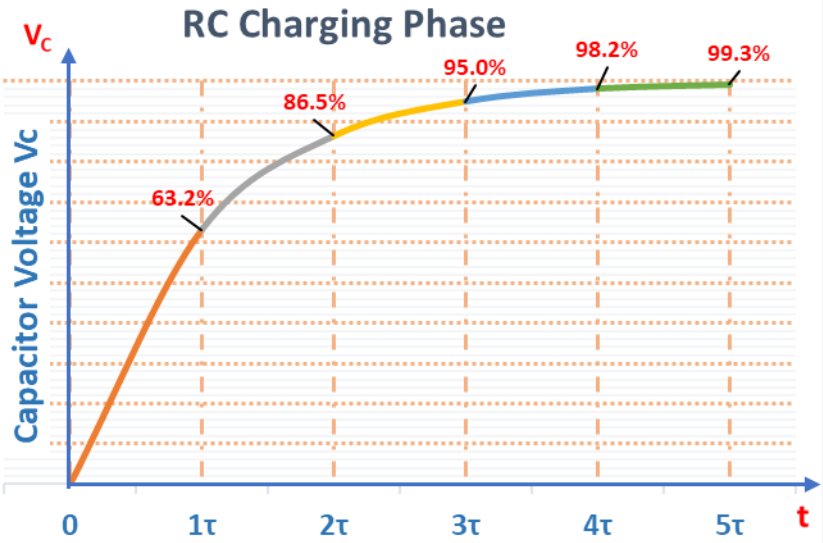


Time Constant τ	Capacitor Current I_C
1τ	$0.368 * \frac{E_S}{R}$
2τ	$0.135 * \frac{E_S}{R}$
3τ	$0.05 * \frac{E_S}{R}$
4τ	$0.018 * \frac{E_S}{R}$
5τ	$0.007 * \frac{E_S}{R}$

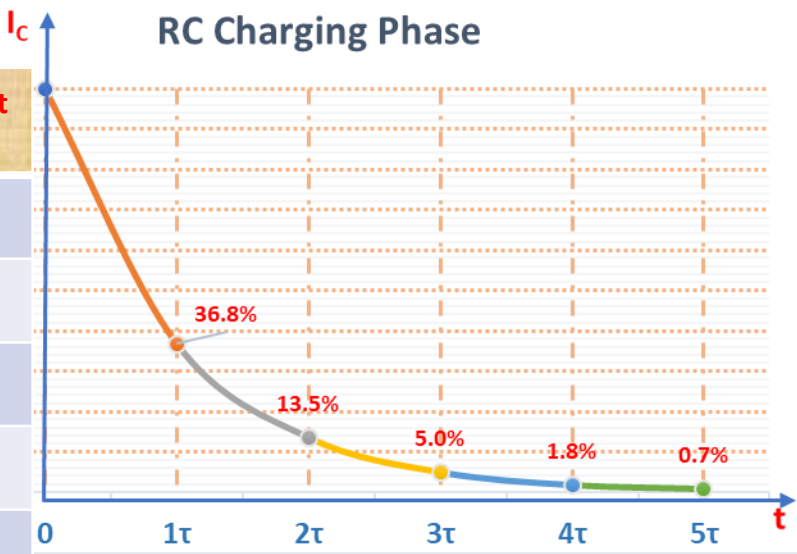


- It takes approximately 5τ to reach its final steady-state value

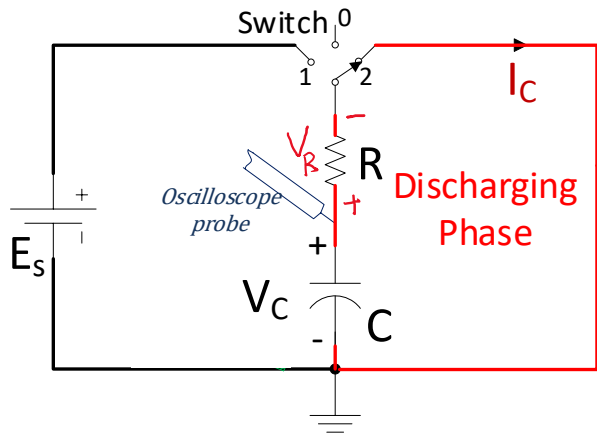Transient curves for series RC circuits - Discharging phase



Time Constant τ	Capacitor Voltage V_C	Resistor Voltage V_R
1τ	$0.368 * E_S$	$0.368 * E_S$
2τ	$0.135 * E_S$	$0.135 * E_S$
3τ	$0.05 * E_S$	$0.05 * E_S$
4τ	$0.018 * E_S$	$0.018 * E_S$
5τ	$0.007 * E_S$	$0.007 * E_S$

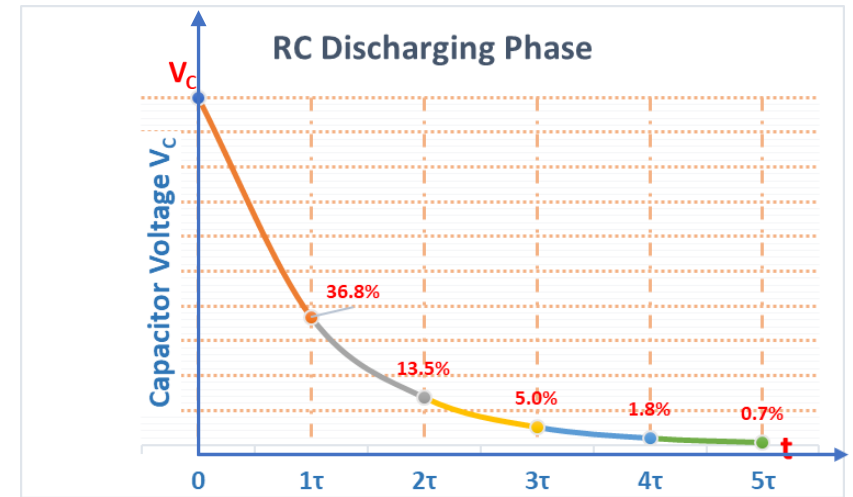

The Time Constant (τ) = $R * C$

Capacitor Voltage V_C

Initial Value = E_S


Final steady Value = 0 V

Capacitor Current I_C

Initial Value = $\frac{E_S}{R}$

Final steady Value = 0 A

Time Constant τ	Capacitor Current I_C
1τ	$0.368 * \frac{E_S}{R}$
2τ	$0.135 * \frac{E_S}{R}$
3τ	$0.05 * \frac{E_S}{R}$
4τ	$0.018 * \frac{E_S}{R}$
5τ	$0.007 * \frac{E_S}{R}$

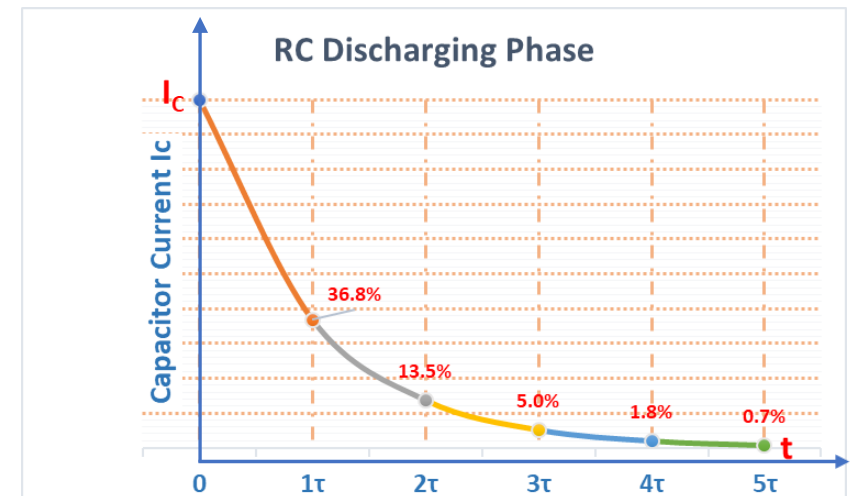

- It takes approximately 5τ to reach its final steady-state value

Inductor


- The inductance of a coil can be approximated from its physical characteristics as

$$L = \mu_m \frac{N^2 A}{l} \text{ (H)}$$

μ_m = permeability of the core, $\text{Wb/At}\cdot\text{m}$


A = cross-sectional area of the core, m^2

l = length of the coil, m

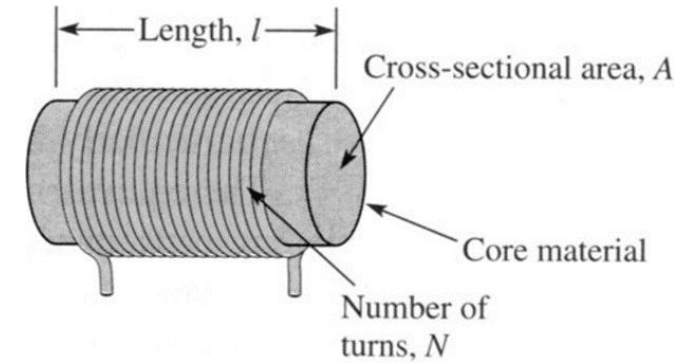


Inductors in series

$$L_T = L_1 + L_2 + L_3$$

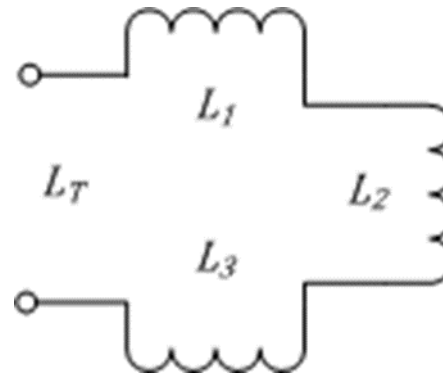


Inductors in parallel

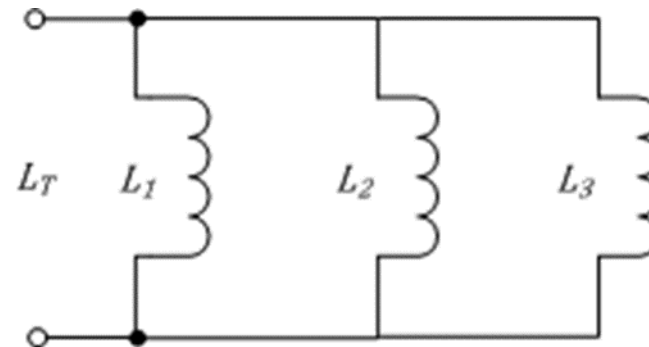
$$L_{EQ} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$



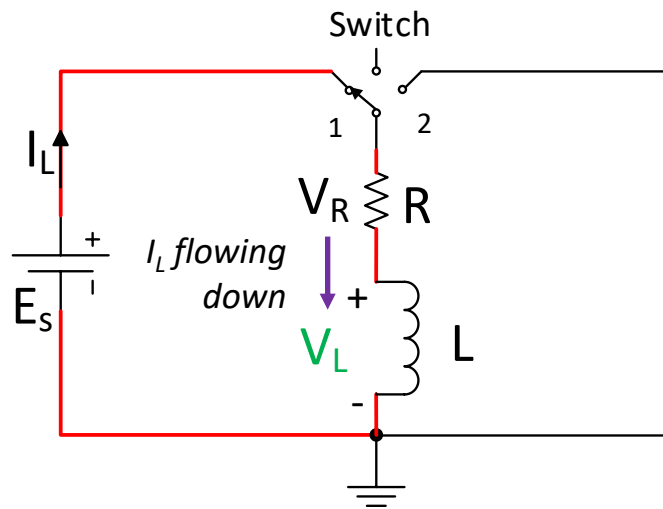Transient curves for series RL circuits - Energizing phase



Time Constant τ	Inductor Current I_L
1τ	$0.632 * \frac{E_S}{R}$
2τ	$0.865 * \frac{E_S}{R}$
3τ	$0.95 * \frac{E_S}{R}$
4τ	$0.982 * \frac{E_S}{R}$
5τ	$0.993 * \frac{E_S}{R}$

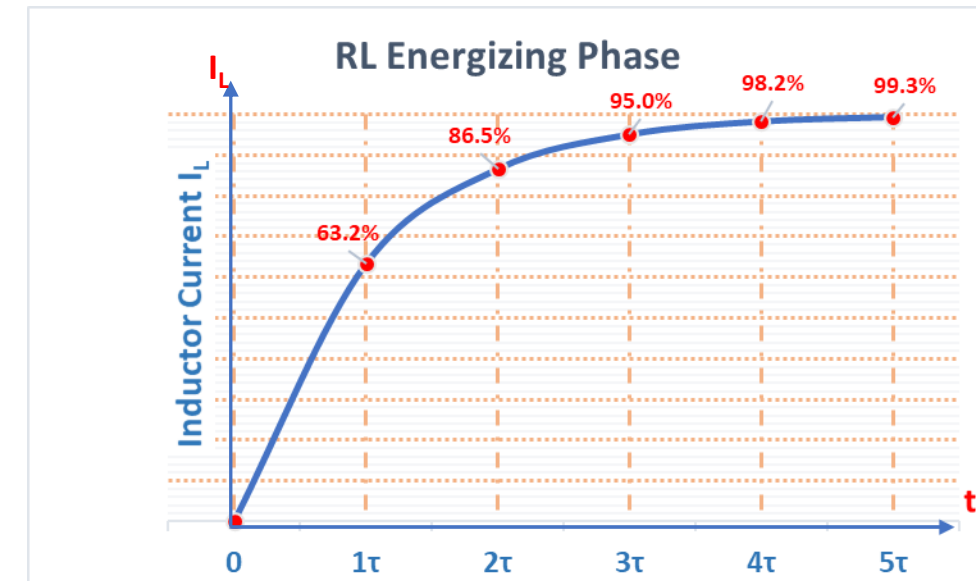

The Time Constant (τ) = $\frac{L}{R}$

Inductor Current I_L

Initial Value = 0 A


Final steady Value = $\frac{E_S}{R}$

Inductor Voltage V_L

Initial Value = E_S


Final steady Value = 0 V

Time Constant τ	Inductor Voltage V_L	Resistor Voltage V_R
1τ	$0.368 * E_S$	$0.632 * E_S$
2τ	$0.135 * E_S$	$0.865 * E_S$
3τ	$0.05 * E_S$	$0.95 * E_S$
4τ	$0.018 * E_S$	$0.982 * E_S$
5τ	$0.007 * E_S$	$0.993 * E_S$

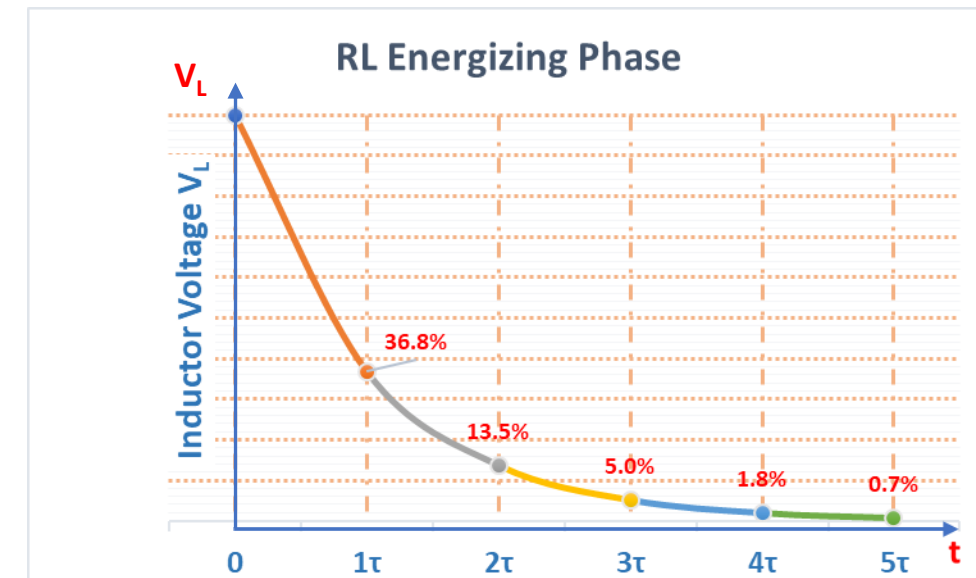

- It takes approximately 5τ to reach its final steady-state value

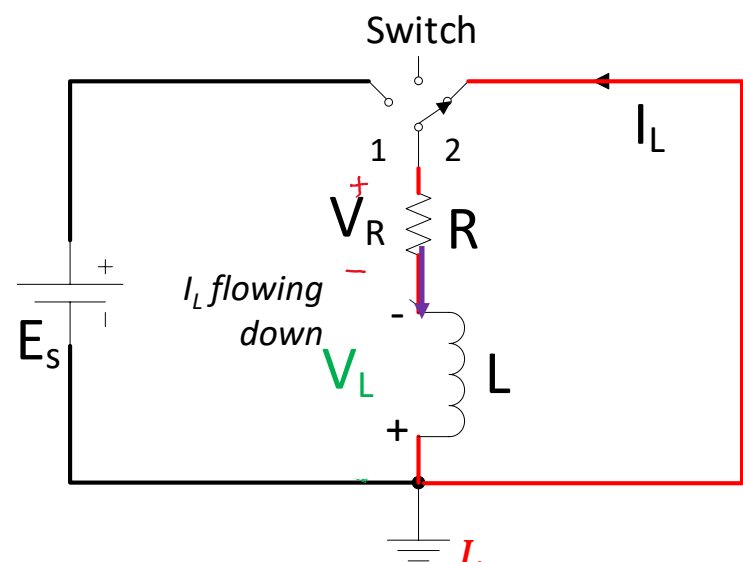Transient curves for series RL circuits — De-energizing phase



The Time Constant (τ) = $\frac{L}{R}$

Inductor Current I_L

Initial Value = $\frac{E_S}{R}$


Final steady Value = 0 A

Inductor Voltage V_L


Initial Value = - E_S

Final steady Value = 0 V

Time Constant τ	Inductor Current I_L
1 τ	$0.368 * \frac{E_S}{R}$
2 τ	$0.135 * \frac{E_S}{R}$
3 τ	$0.05 * \frac{E_S}{R}$
4 τ	$0.018 * \frac{E_S}{R}$
5 τ	$0.007 * \frac{E_S}{R}$

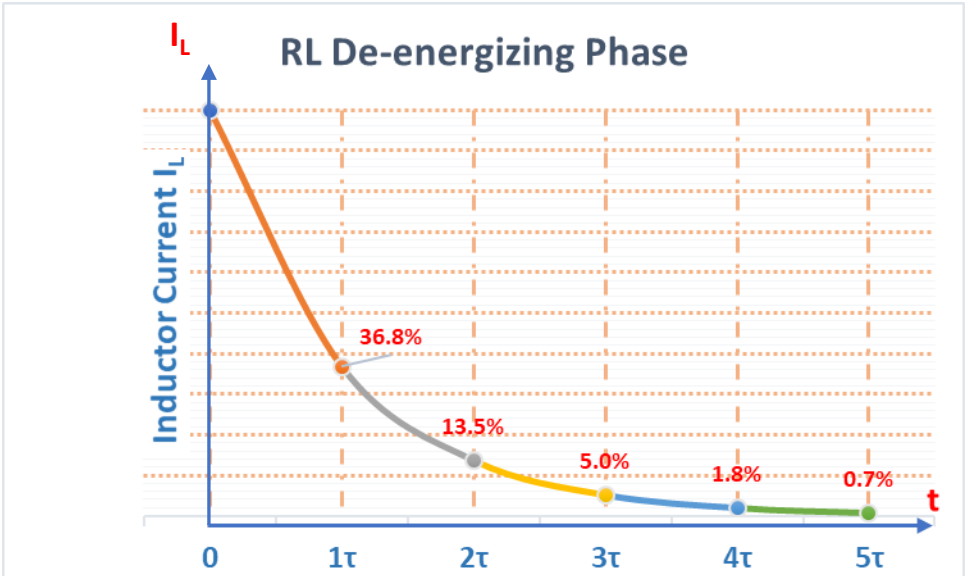

Time Constant τ	Inductor Voltage V_L	Resistor Voltage V_R
1 τ	- 0.368* E_S	0.368* E_S
2 τ	- 0.135* E_S	0.135* E_S
3 τ	- 0.05* E_S	0.05* E_S
4 τ	- 0.018* E_S	0.018* E_S
5 τ	- 0.007* E_S	0.007* E_S

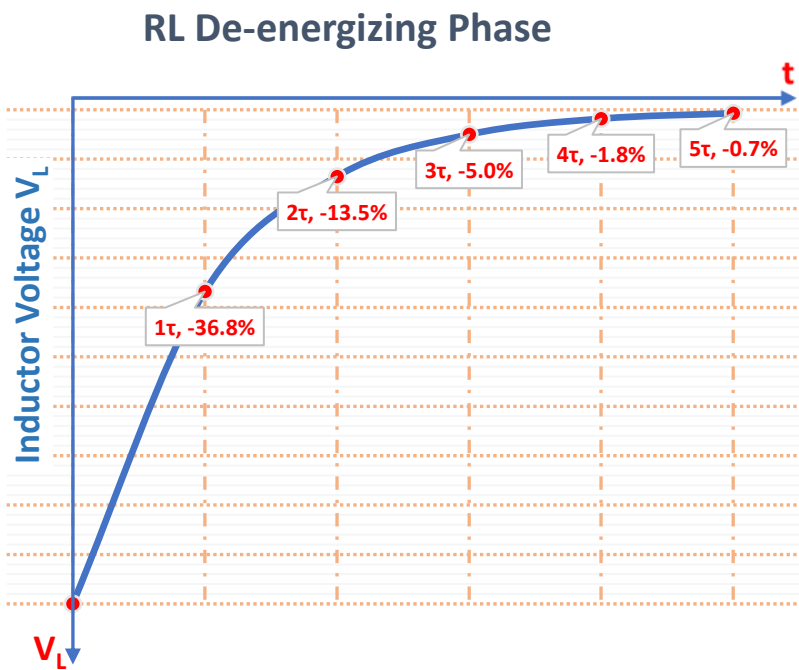


Note : The inverted V_L , also term as “Back EMF” reduces its strength as the magnetic energy collapses gradually.
The current falls exponentially to zero with the decay in the magnetic field

Capacitor - C

Capacitive Reactance – X_C

➤ $X_C(\Omega) = \frac{1}{2\pi f c}$

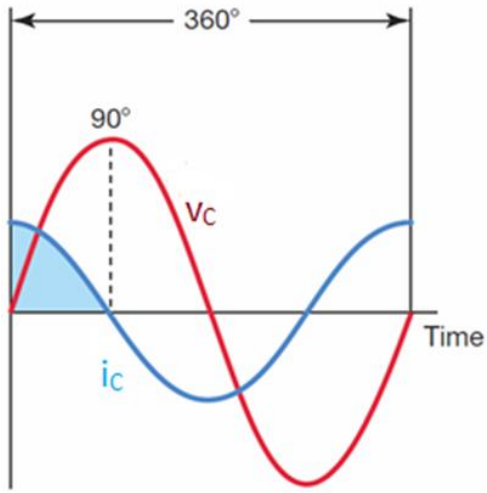
- ❖ The **current** i_c **leads** the **voltage** v_c in the ideal **capacitor** by **90°**
- ❖ Current through X_C , $i_c = v_c / x_c$



ICE

Current – Capacitor - Voltage


Impedance – z (Ω)

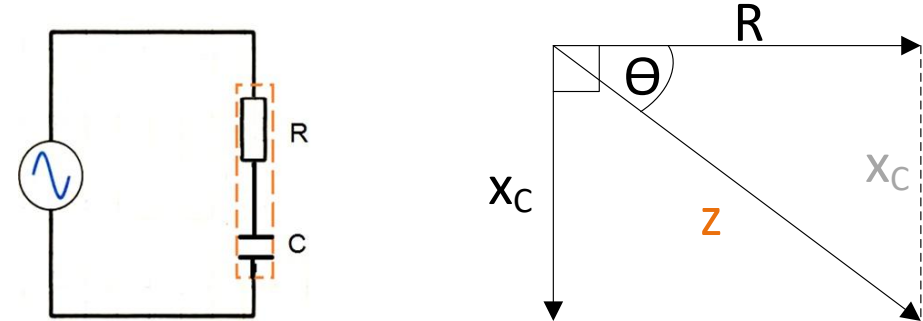

Formula for Impedance, z (Ω):

- Magnitude of z (Ω): $|Z| = \sqrt{R^2 + x_C^2}$
- $z = \sqrt{R^2 + x_C^2} \angle \theta^\circ (\Omega)$
- $\theta^\circ = \tan^{-1} \left(-\frac{x_C}{R} \right)$


Series RC Circuit

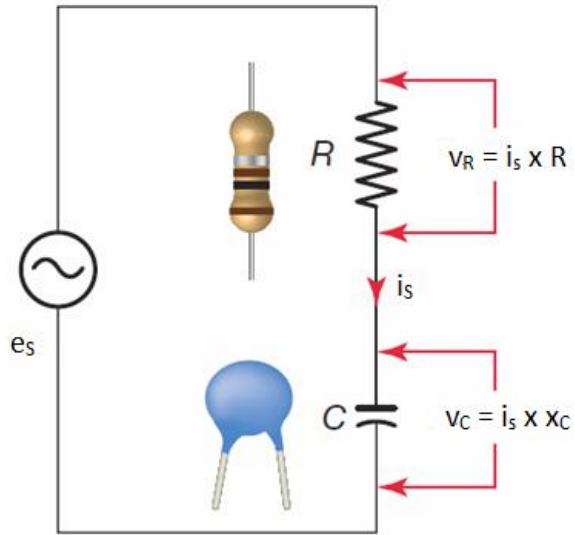


$$i_s = \frac{e_s}{Z}$$

$$V_R = i_s \times R$$

$$V_C = i_s \times X_C$$

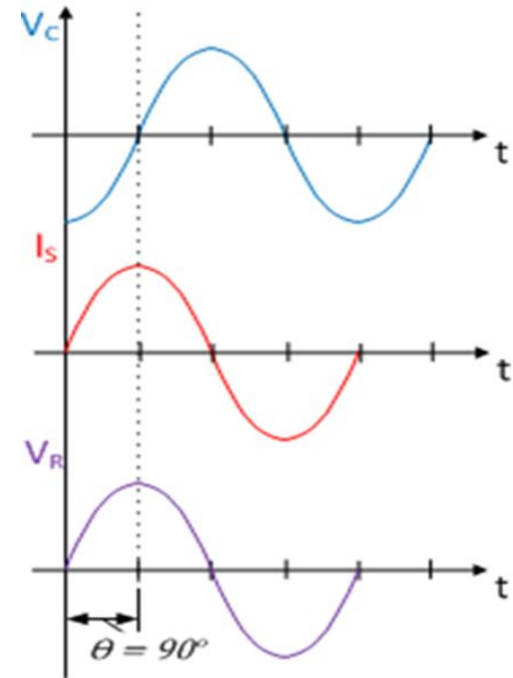

Voltage phasor diagram

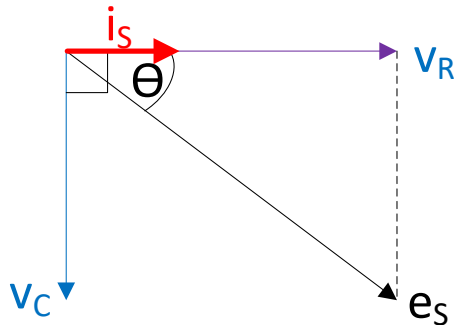

- For Capacitor → Current, i_s leads voltage, v_c by **90°**
- For Resistor → Current, i_s is always in phase with voltage V_R .

$$e_s = \sqrt{v_R^2 + v_C^2} \angle \theta^\circ \text{ (V)}$$

$$\text{where } \theta^\circ = \tan^{-1} \left(-\frac{x_C}{R} \right)$$

EXAMPLE 17-14

Problem:

For the series RC circuit shown in  **Figure 17-29**:

- Calculate the value of the current flow.
- Calculate the value of the voltage drop across the resistor.
- Calculate the value of the voltage drop across the capacitor.
- Calculate the circuit phase angle based on the voltage drops across the resistor and capacitor.
- Express all voltages in polar notation.

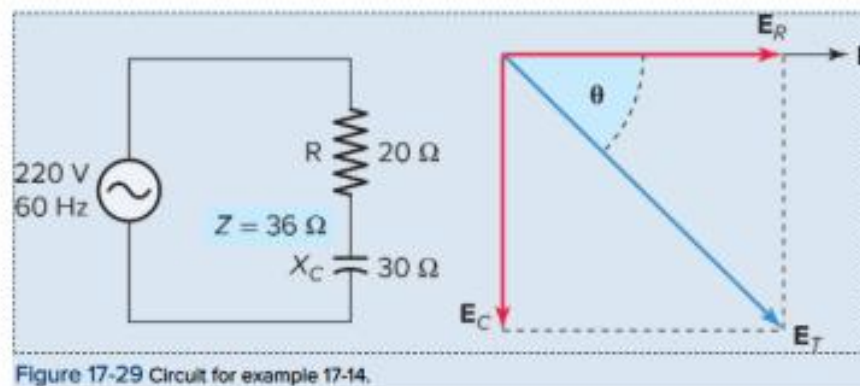


Figure 17-29 Circuit for example 17-14.

Solution:

a.
$$I = \frac{E_T}{Z}$$
$$= \frac{220 \text{ V}}{36 \Omega}$$
$$= 6.11 \text{ A}$$

b.
$$E_R = I \times R$$
$$= 6.11 \text{ A} \times 20 \Omega$$
$$= 122 \text{ V}$$

c.
$$E_C = I \times X_C$$
$$= 6.11 \text{ A} \times 30 \Omega$$
$$= 183 \text{ V}$$

d.
$$\theta = \tan^{-1} \frac{E_C}{E_R}$$
$$= \tan^{-1} \frac{183}{122}$$
$$= \tan^{-1}(1.5)$$
$$= 56.31^\circ$$

The calculated circuit phase angle is the same as that determined in the previous example using the ratio of X_C/R .


e.
$$E_T = 220 \text{ V} \angle -56.31^\circ$$
$$E_R = 122 \text{ V} \angle 0^\circ$$
$$E_C = 183 \text{ V} \angle -90^\circ$$

Inductor – L

Inductive Reactance – X_L



➤ $X_L(\Omega) = 2\pi fL$

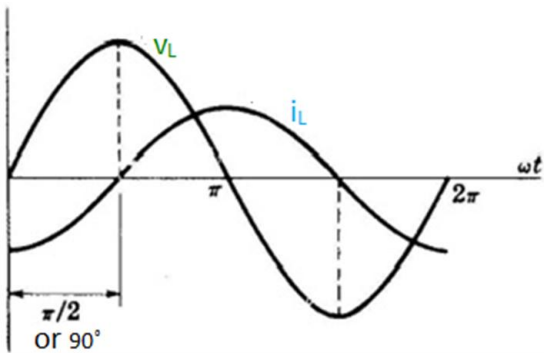- ❖ In a purely inductive circuit, i_L always lag the voltage V_L by 90° or $\pi/2$.
- ❖ Current through X_L , $i_L = v_L / x_L$



Voltage – Inductor - Current

Impedance – z (Ω)

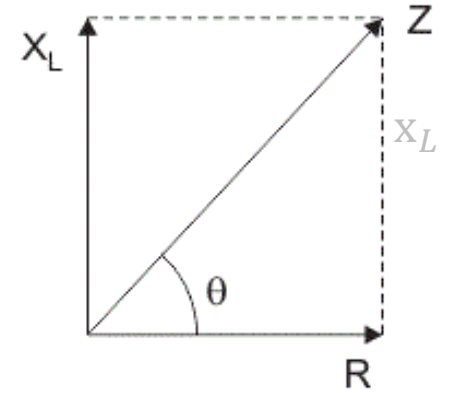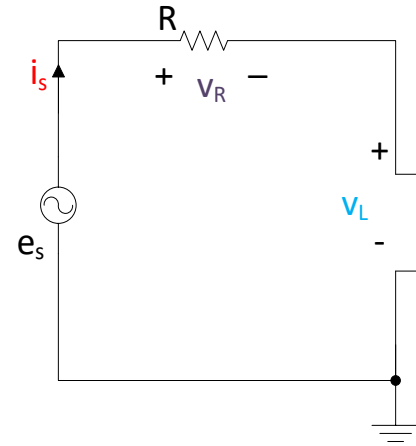

Formula for Impedance, z (Ω):

- Magnitude of z (Ω): $|Z| = \sqrt{R^2 + x_L^2}$
- $z = \sqrt{R^2 + x_L^2} \angle \theta^\circ$ (Ω)
- $\theta^\circ = \tan^{-1} \left(\frac{x_L}{R} \right)$

EXAMPLE 17-9


Problem:

An AC series RL circuit is made up of a resistor that has a resistance value of $150\ \Omega$ and an inductor that has an inductive reactance value of $100\ \Omega$. Calculate the impedance and the phase angle theta (θ) of the circuit.

Solution:

$$\begin{aligned} Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{150^2 + 100^2} \\ &= \sqrt{32,500} \\ &= 180\ \Omega \\ \theta &= \tan^{-1} \left(\frac{X_L}{R} \right) \\ &= \tan^{-1} \left(\frac{100}{150} \right) \\ &= \tan^{-1} (0.667) \\ &= 33.7^\circ \end{aligned}$$


Series RL Circuit

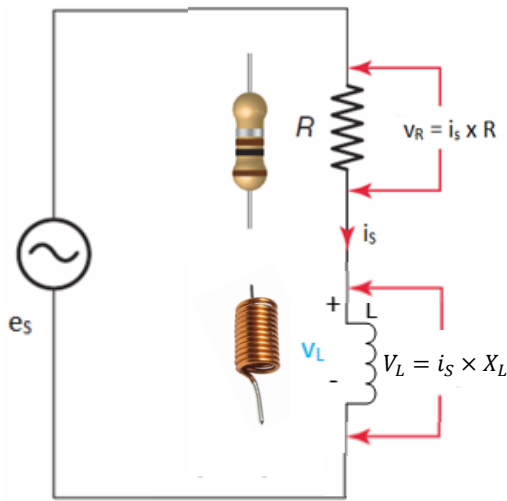


$$i_s = \frac{e_s}{Z}$$

$$V_R = i_s \times R$$

$$V_L = i_s \times X_L$$

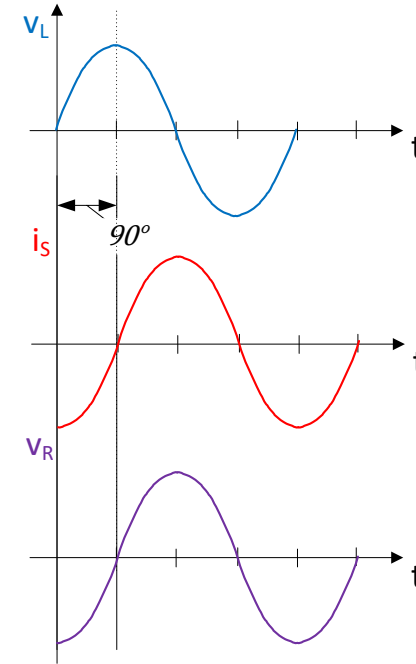

Voltage phasor diagram

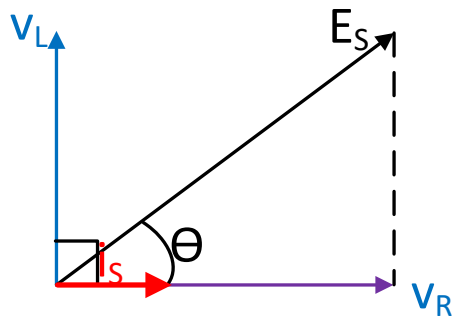

- For Inductor → Current, i_s lags voltage, v_L by **90°**
- For Resistor → Current, i_s is always in phase with voltage V_R .

$$e_s (V) = \sqrt{v_R^2 + v_L^2} \angle \theta^\circ$$

where $\theta^\circ = \tan^{-1} \left(\frac{x_L}{R} \right)$

EXAMPLE 17-10

Problem:

For the series RL circuit shown in  Figure 17-17:

- Calculate the value of the current flow.
- Calculate the value of the voltage drop across the resistor.
- Calculate the value of the voltage drop across the inductor.
- Calculate the circuit phase angle based on the voltage drops across the resistor and inductor.
- Express all voltages in polar notation.

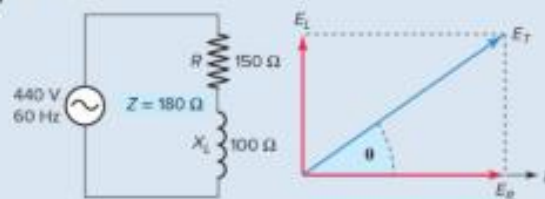


Figure 17-17 RL series circuit for example 17-10.

Solution:

- $$I = \frac{E_T}{Z}$$

$$= \frac{440 \text{ V}}{180 \Omega}$$

$$= 2.44 \text{ A}$$
- $$E_R = I \times R$$

$$= 2.44 \text{ A} \times 150 \Omega$$

$$= 366 \text{ V}$$
- $$E_L = I \times X_L$$

$$= 2.44 \text{ A} \times 100 \Omega$$

$$= 244 \text{ V}$$
- $$\theta = \tan^{-1} \frac{E_L}{E_R}$$

$$= \tan^{-1} \frac{244 \text{ V}}{366 \text{ V}}$$

$$= \tan^{-1} (0.667)$$


$$= 33.7^\circ$$
- $$E_T = 440 \text{ V} \angle 33.7^\circ$$

$$E_R = 366 \text{ V} \angle 0^\circ$$

$$E_L = 244 \text{ V} \angle 90^\circ$$


Question a) Describe the phase relationship between V_{R1} and I_{R1}

Q3


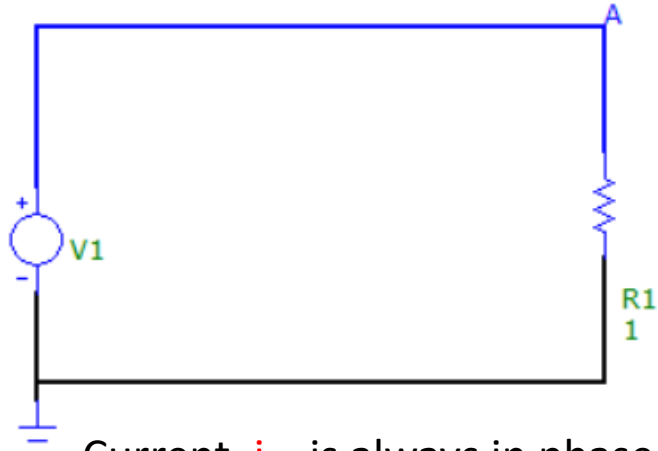


Current, i_{R1} is always in phase with voltage V_R .


XC_ACcircuit.cir

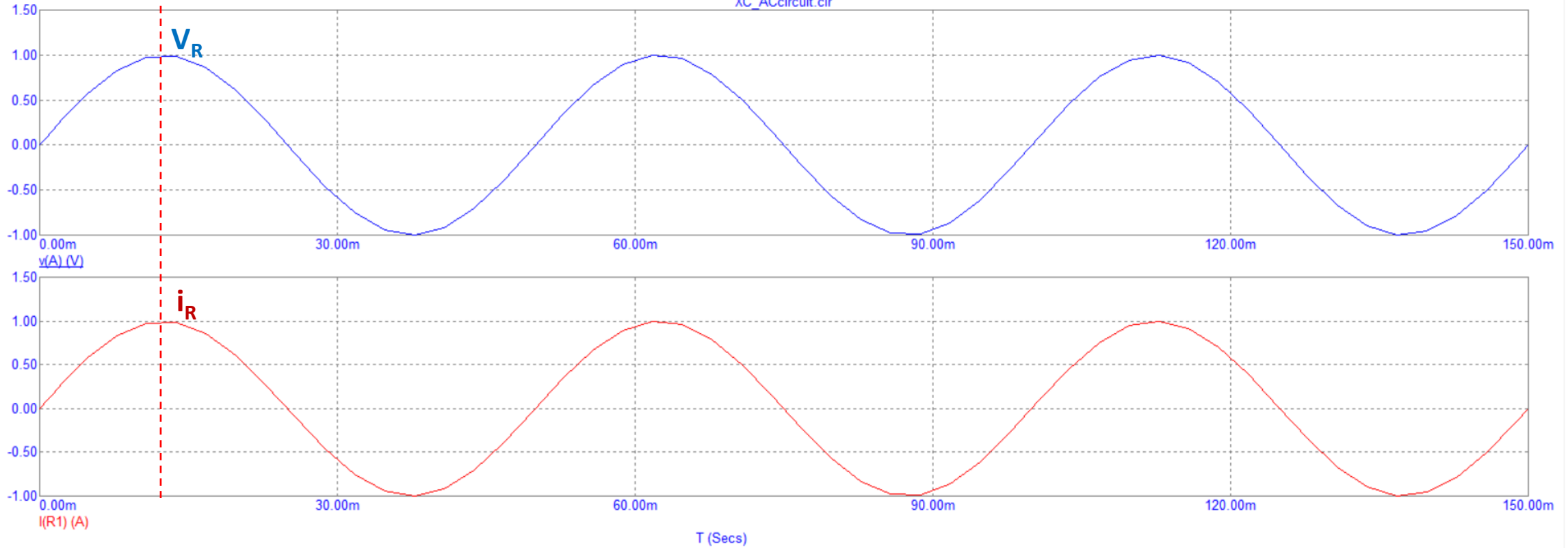

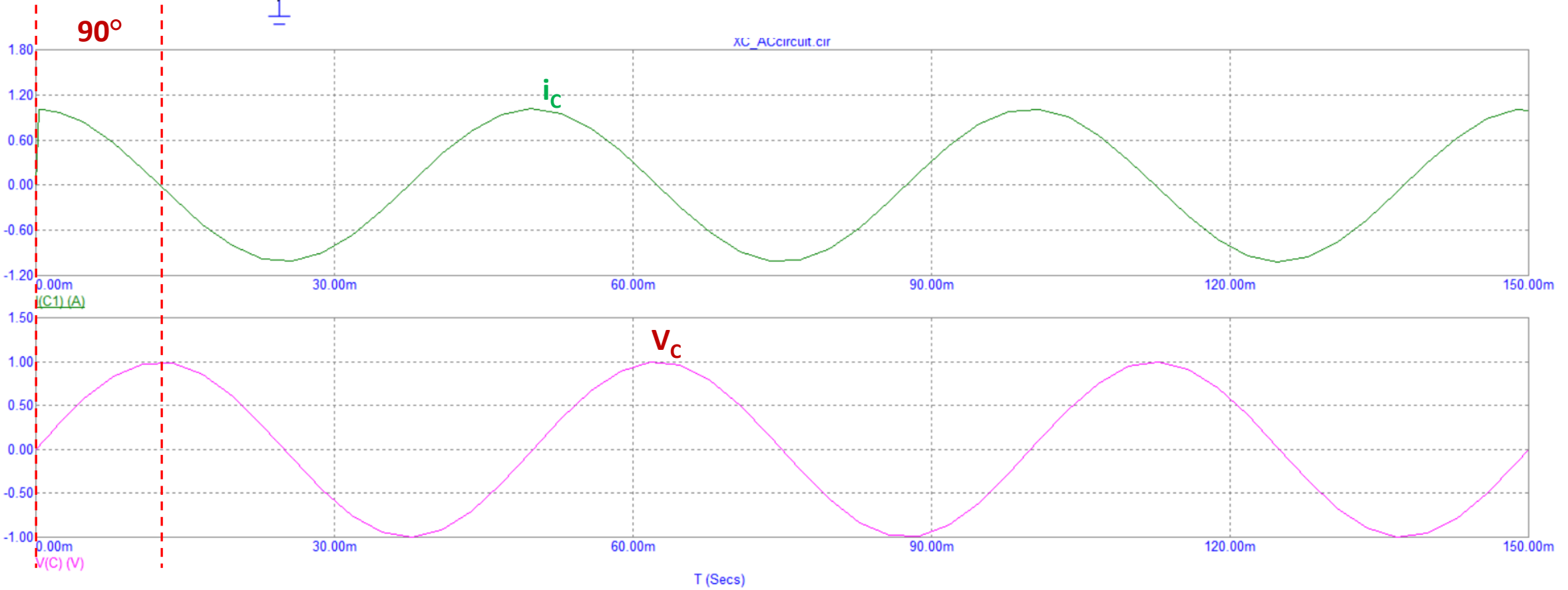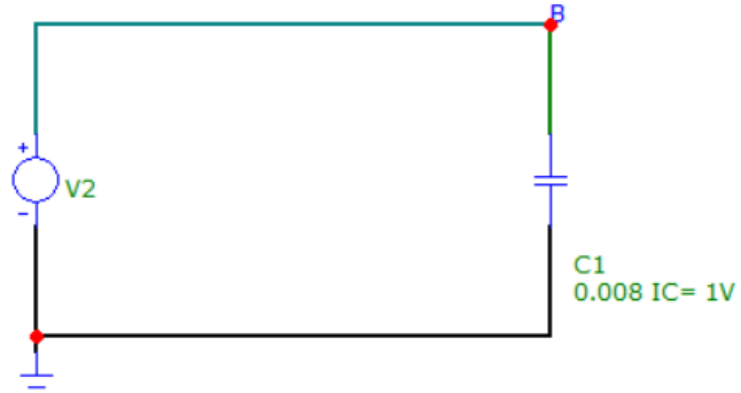Question b) Describe the phase relationship between V_{C1} and I_{C1}



Diode

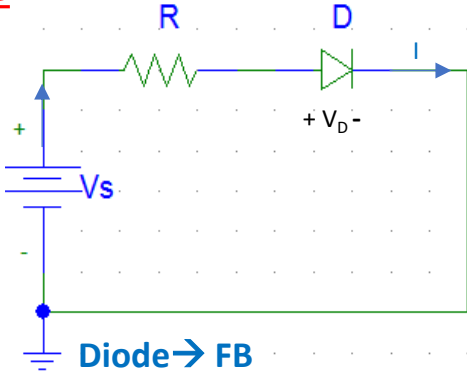


Diode $\rightarrow$ FB

$$V_D = V_t = (0.7V)$$

$$I = \frac{V_s - V_D}{R}$$

$$\text{Power (Diode)} = I \times V_D$$

$$\text{Power (Resistor)} = I^2 R$$

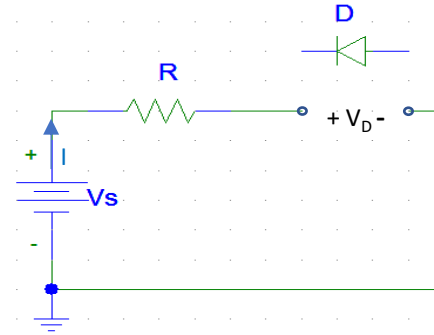

Diode $\rightarrow$ RB $\rightarrow$ Diode is considered Open


$$V_D = V_s$$

$$I = 0$$

Power dissipation for diode

$$P = VI \text{ only}$$

Don't use $I^2 R$ or V^2 / R

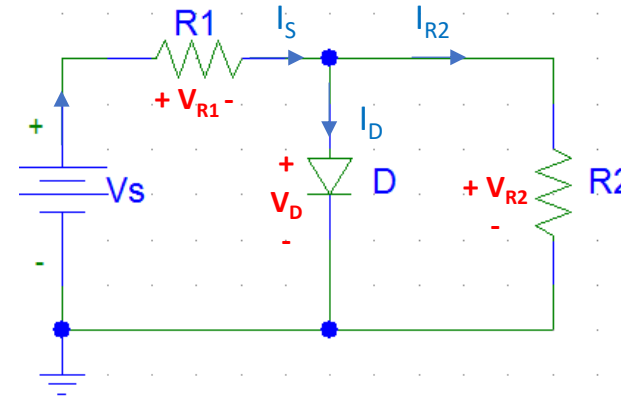


Diode $\rightarrow$ Forward Bias, $V_D = V_t = (0.7V)$

$$I_s = \frac{V_s - V_D}{R_1}, \quad I_{R2} = \frac{V_D}{R_2}$$

$$I_D = I_s - I_{R2}$$

$$\text{Power (Diode)} = I_D \times V_D$$

$$\text{Power (Resistor)} = I_s^2 R$$

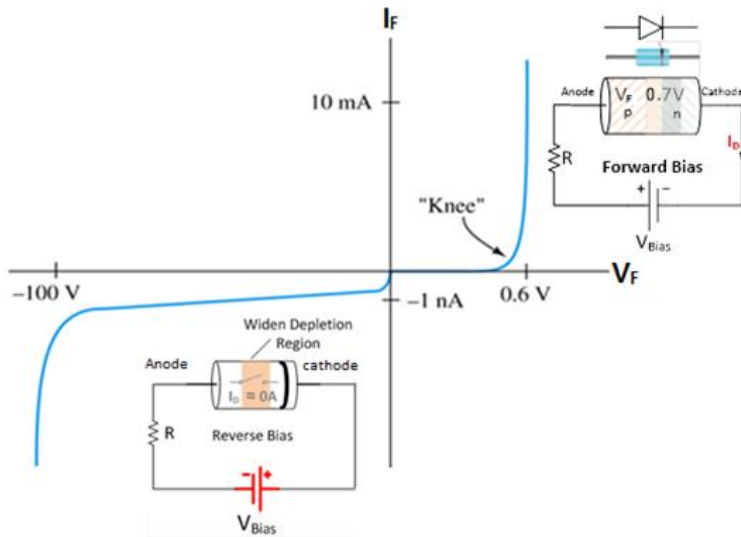

Zener Diode

Zener Diodes (unlike normal Diodes) are operated in **reverse biased condition** and used for voltage regulation.

Forward Bias (Fig 1) → Voltage across Zener diode = $V_D = 0.7V$ (Same as normal Diode)

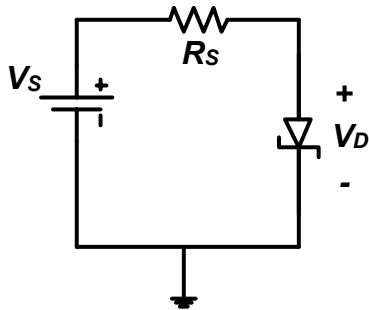


Fig 1


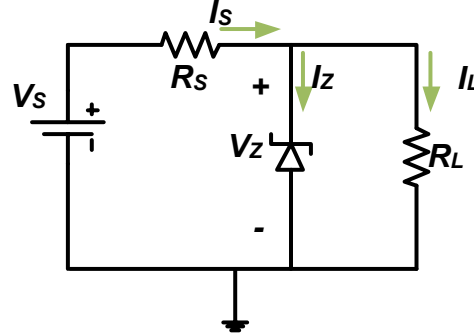


Fig 2


Reverse Bias (Fig 2) → If $V_s > V_Z$ and $I_{ZK} < I_Z < I_{ZM}$, then voltage across Zener Diode = V_Z

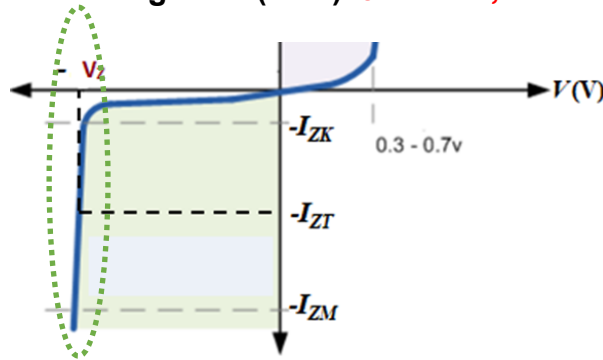From Fig 2--→ (KCL) $I_s = I_Z + I_L$, $I_L = V_Z/R_L$, $I_s = (V_s - V_Z)/R_s$



Zener Diode -

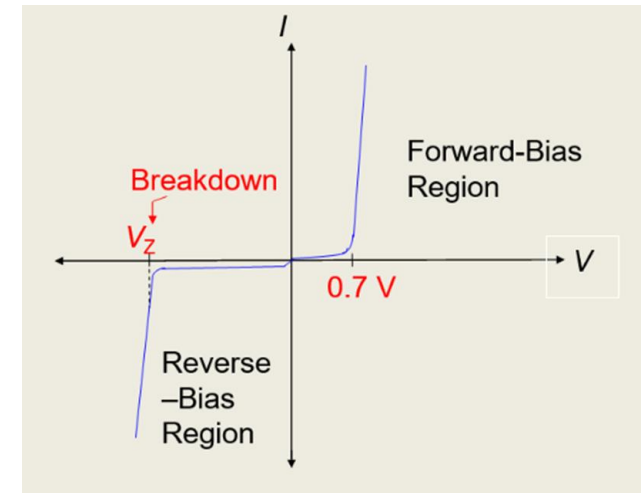
I-V Characteristic in **Breakdown Region**



- Zener diodes are specifically used in applications where the **reverse-breakdown region** is the desired operating region.
- If $I_Z < I_{ZK}$, Zener is **reverse biased** but **not breakdown**, Hence V_Z cannot be stabilized at a constant value.
- If $I_Z > I_{ZM}$, Zener diode **may be damaged** due to excessive power!

Selection of current limiting resistor, R_S

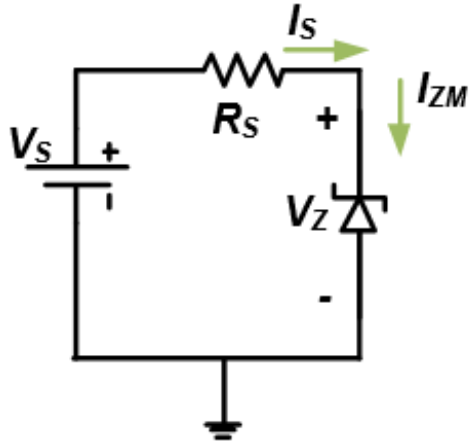To find minimum R_S to keep $I_Z < I_{ZM} \rightarrow$ The condition $R_L = \infty$ (open, No Load) & $I_Z = I_{ZM}$




$$I_S = I_Z = I_{ZM}$$

$$I_S = \frac{V_S - V_Z}{R_{S(min)}}$$

$$R_{S(min)} = \frac{V_S - V_Z}{I_S}$$

If R_S and R_L values are given,

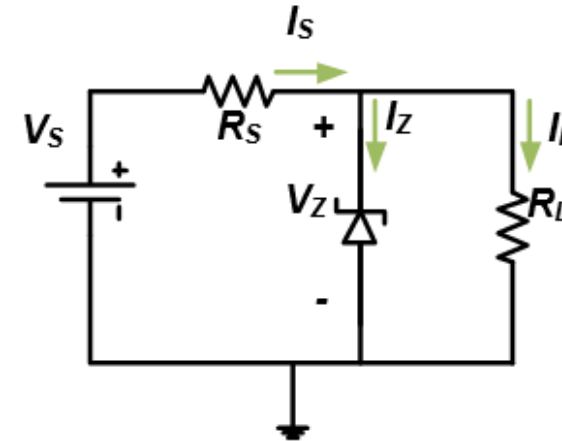


$$\begin{aligned} KCL \rightarrow I_S &= I_Z + I_L \\ I_S &= \frac{V_S - V_Z}{R_S} \\ I_L &= \frac{V_Z}{R_L} \\ I_Z &= I_S - I_L \end{aligned}$$

If $I_{ZK} < I_Z < I_{ZM}$, Zener Diode is functioning as Voltage Regulator.




- If $I_Z < I_{ZK}$, V_Z cannot be stabilized at a constant value. Zener Diode will not function as Voltage regulator.
- If $I_Z > I_{ZM}$, Zener diode **may be damaged** due to excessive power!

DC Power Supply: Transformer

STEP-DOWN TRANSFORMER

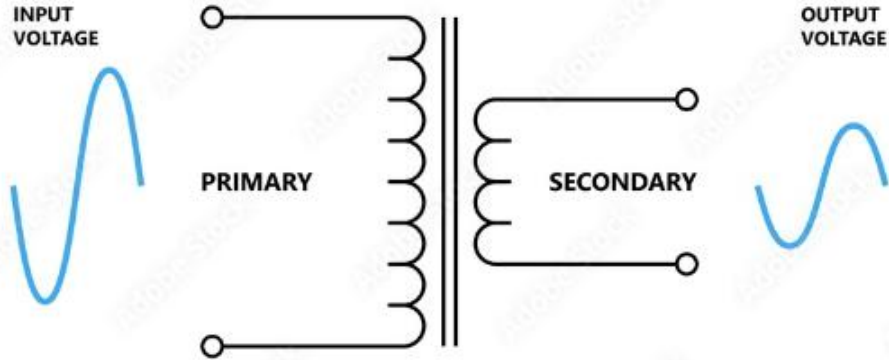


STEP-UP TRANSFORMER

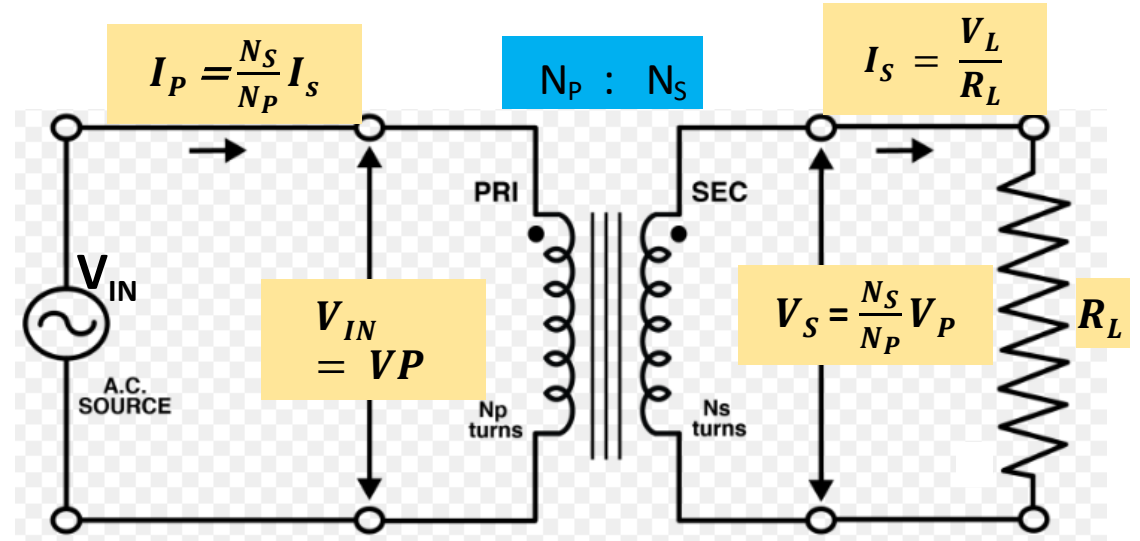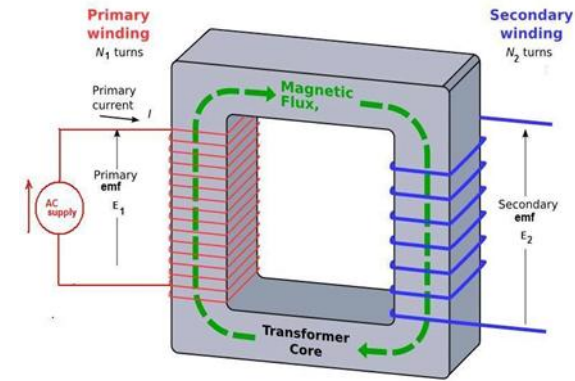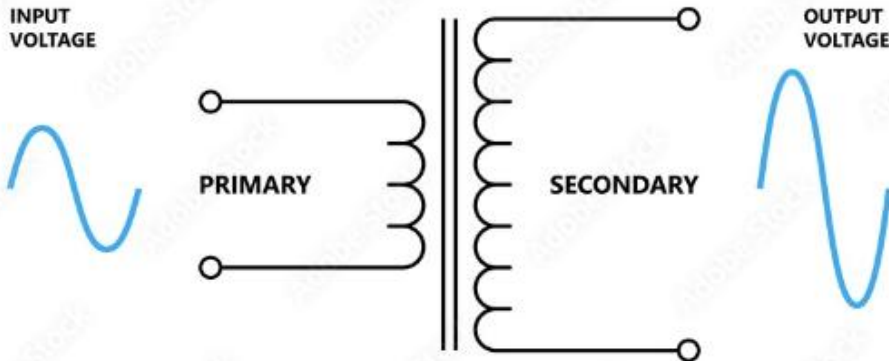

Schematic Symbol

$$(\text{turn ratio}) n = \frac{V_P}{V_S} = \frac{N_P}{N_S} = \frac{I_S}{I_P}$$


Half Wave Rectifier

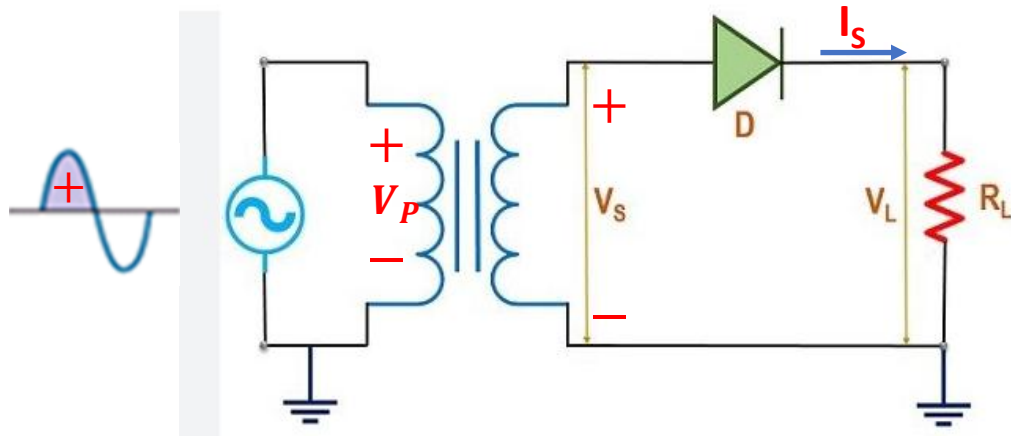

During the positive half-cycle, D_1 is **forward** biased.


KVL $\rightarrow V_S = V_D + V_L$, where $V_D = 0.7V$.
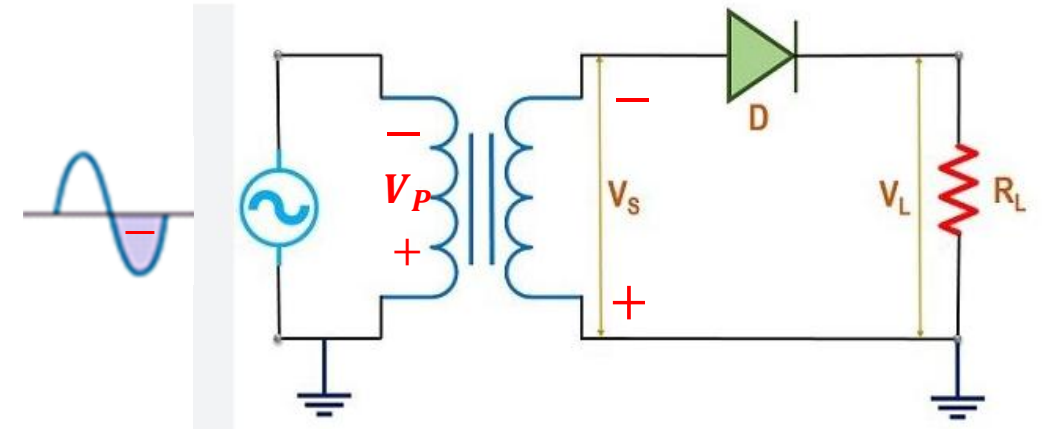
$$I_S = \frac{V_S - V_D}{R_L}, V_L = I_L \times R_L$$





During the negative half-cycle, D_1 is **reverse** biased.


$$I_S = 0, V_L = 0$$

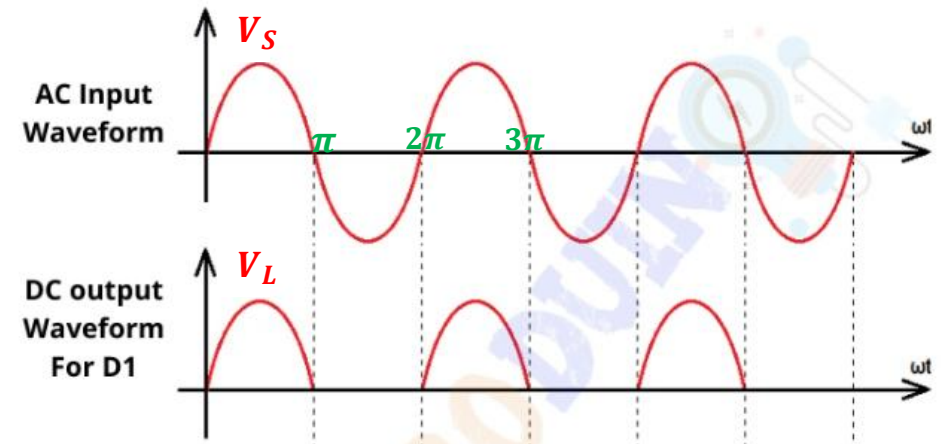

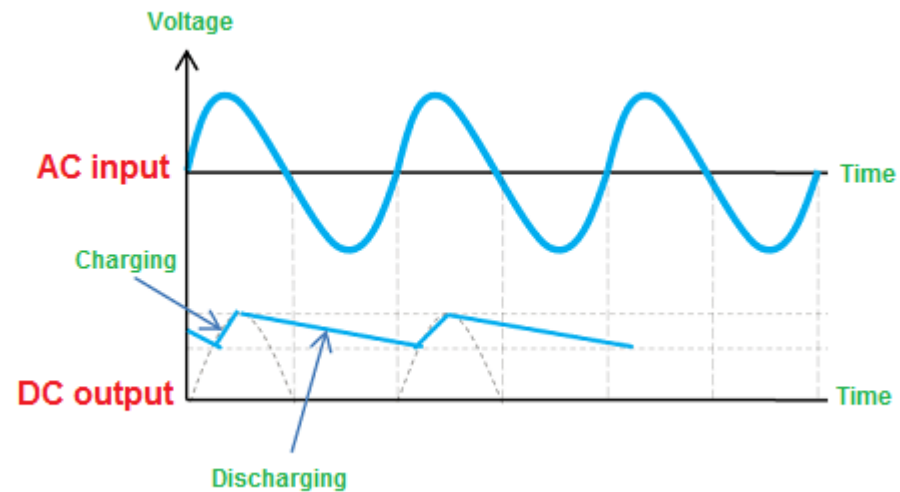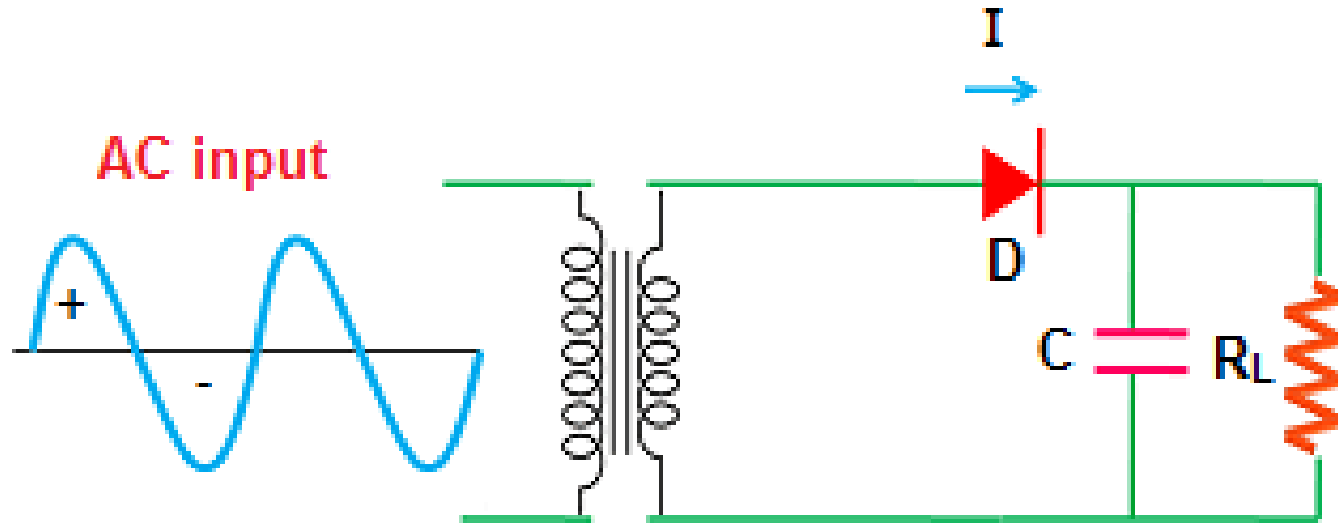Half Wave Rectifier with Capacitor Filter




Full Wave Rectifier

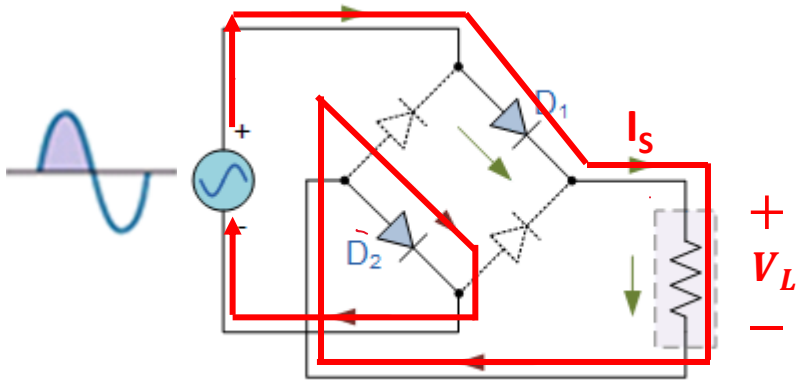

During the positive half-cycle, D_1 & D_2 are **forward** biased and D_3 & D_4 are **reverse** biased.

$$\text{KVL} \rightarrow V_S = V_{D1} + V_{D2} + V_L,$$

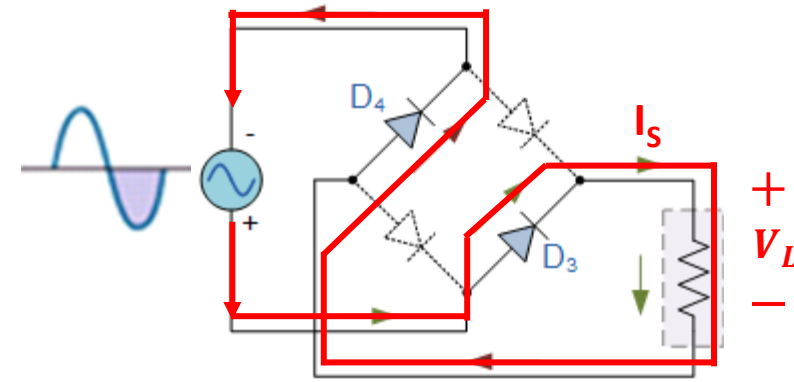
$$I_S = \frac{V_S - 2V_D}{R_L}, V_L = I_L \times R_L$$



During the positive half-cycle, D_1 & D_2 are **forward** biased and D_3 & D_4 are **reverse** biased.

$$\text{KVL} \rightarrow V_S = V_{D3} + V_{D4} + V_L,$$

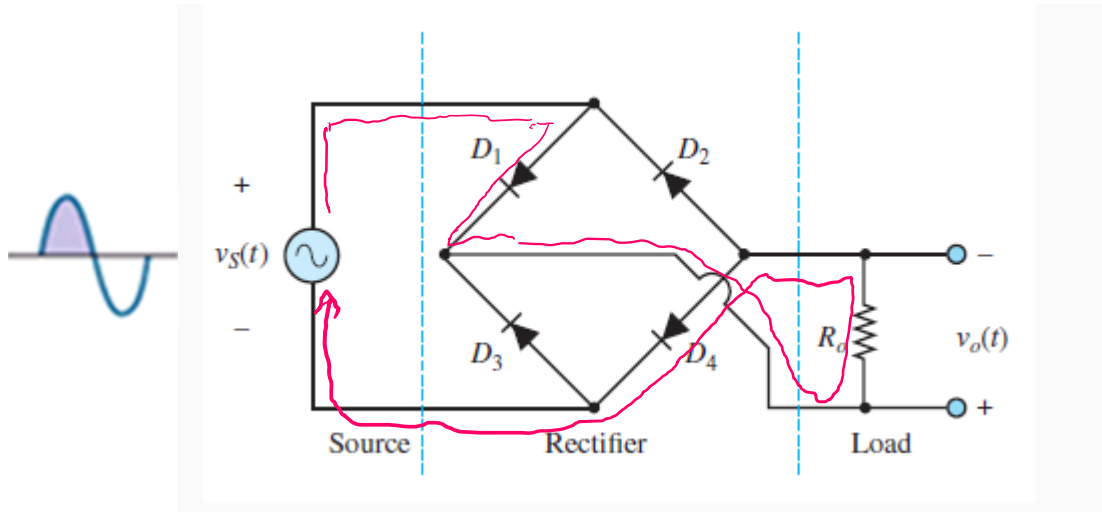
$$I_S = \frac{V_S - 2V_D}{R_L}, V_L = I_L \times R_L$$



During the positive half-cycle, D_1 & D_4 are **forward** biased and D_3 & D_2 are **reverse** biased.

$$\text{KVL} \rightarrow V_S = V_{D1} + V_{D4} + V_o,$$
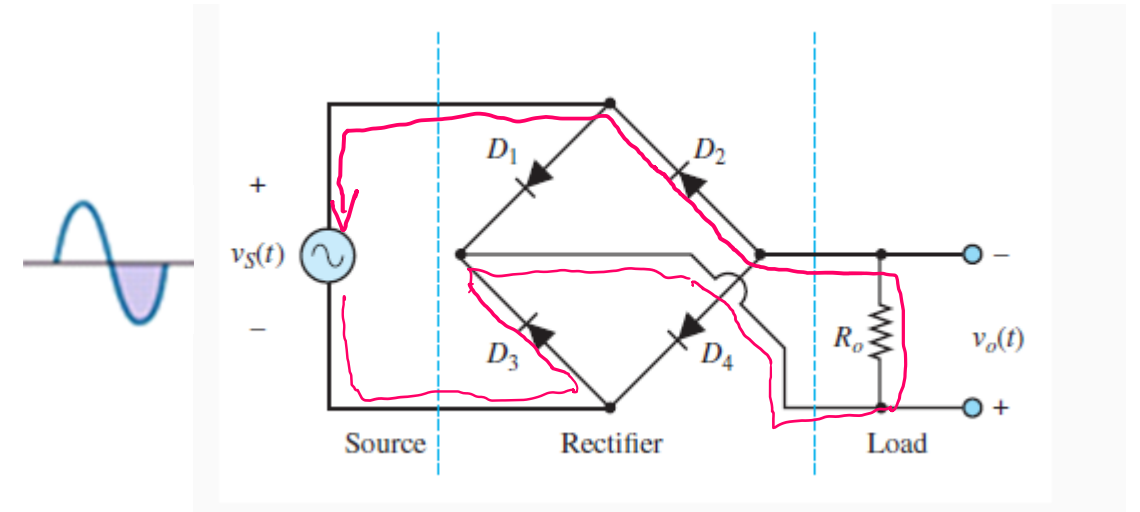
$$I_S = \frac{V_S - 2V_D}{R_o}, V_o = I_L \times R_o$$






During the positive half-cycle, D_2 & D_4 are **forward** biased and D_3 & D_1 are **reverse** biased.

$$\text{KVL} \rightarrow V_S = V_{D3} + V_{D2} + V_L,$$

$$I_S = \frac{V_S - 2V_D}{R_L}, V_o = I_L \times R_L$$

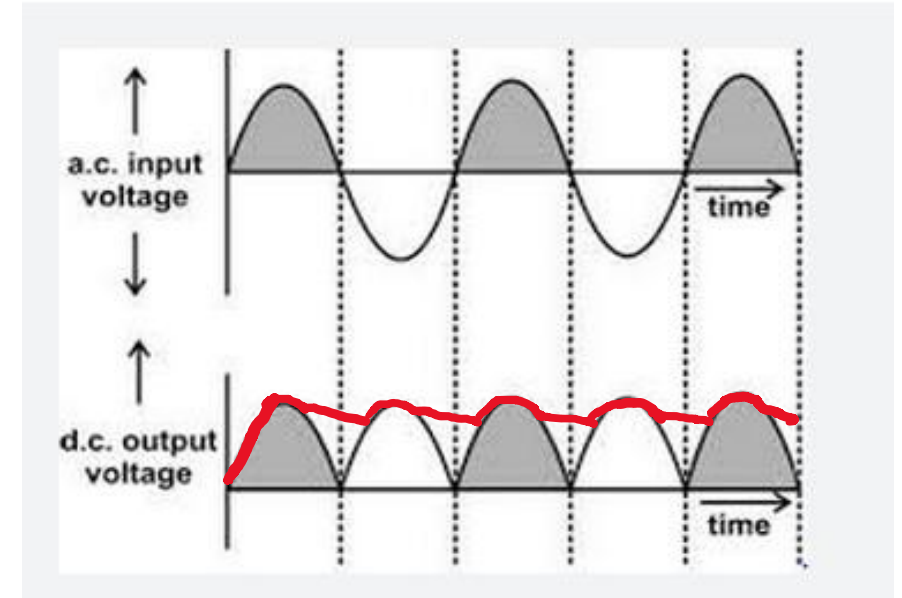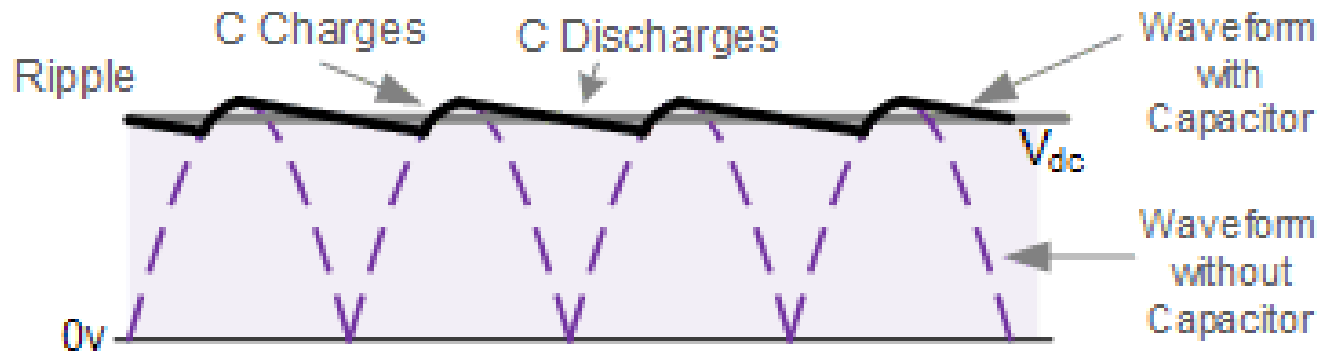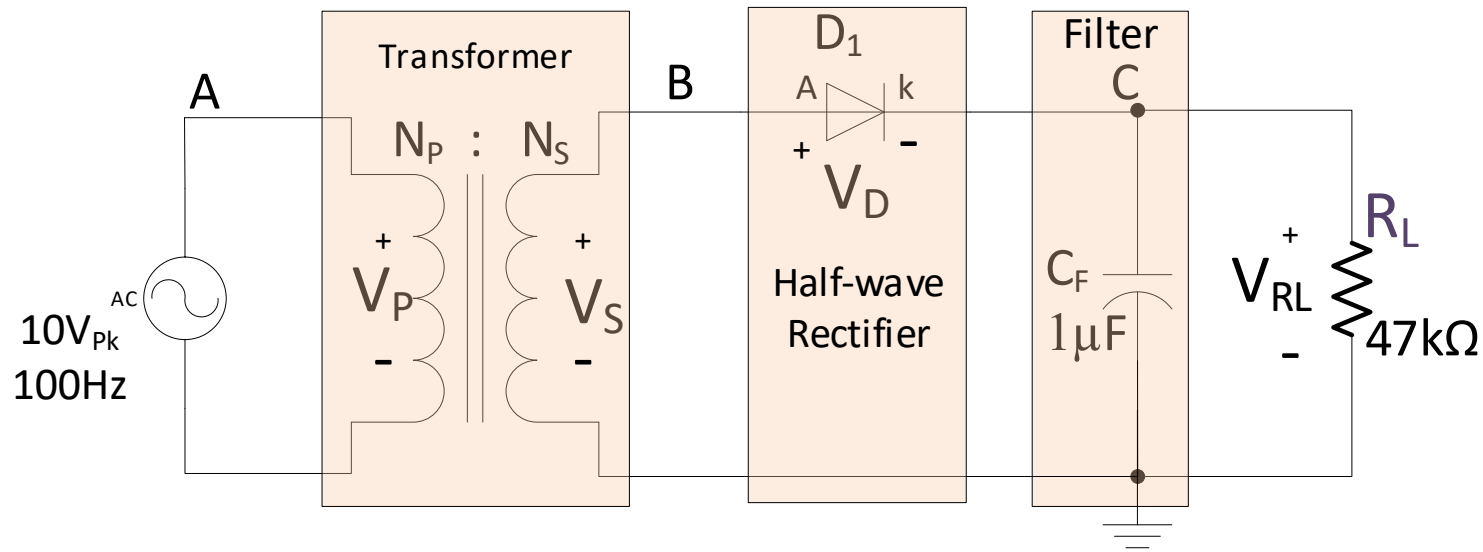Effects of Filter Capacitor and Resistive load



Voltage Regulator

